

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 51645

B.E./B.Tech. DEGREE EXAMINATION, MAY/JUNE 2016

Second Semester

Civil Engineering

**GE 2151 / 10133 EE 206/EE 1153/EE 26/080280011 – BASIC ELECTRICAL AND
ELECTRONICS ENGINEERING**

(Common to all Branches)

(Regulations 2008/2010)

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions.

PART – A (10 × 2 = 20 Marks)

1. Two resistances of 4Ω and 6Ω are connected in parallel across 10 V battery. Determine the current through 6Ω resistance.
2. Define RMS value.
3. Define voltage regulation of a transformer.
4. Why is starter necessary for a dc motor ?
5. Compare PN junction diode and Zener diode.
6. What is effect of saturation of a transistor ?
7. Define Flip-Flop.
8. What are the different sources of errors in DAC ?

9. As related to amplitude modulation, what is overmodulation, undermodulation and 100% modulation ?
10. Why are digital signals said to be noise immune ?

PART – B (5 × 16 = 80 Marks)

11. (a) (i) Explain the working of Single-Phase Energy Meter with necessary diagram. (8)
- (ii) Calculate the
- (1) Form Factor and
- (2) Peak Factor of a full wave rectified sine wave. (8)

OR

- (b) (i) Explain the operation of attraction type of M.I instrument. (8)
- (ii) Explain the working of Dynamometer type wattmeter with necessary diagram. (8)
12. (a) Explain the construction and working principle of DC generator with neat diagram. (16)

OR

- (b) Explain the working principle of various types of Single Phase (1 ϕ) Induction Motor with neat diagram. (16)
13. (a) (i) With neat diagrams, explain how a voltage regulator circuit regulates the output voltage under the following conditions :
- (1) Load resistance increases (4)
- (2) Input voltage decrease (4)
- (ii) (1) Using the two diode analogy, explain why the base-emitter junction has to be forward biased to provide collector current.
- (2) Sketch a common emitter amplifier circuit with an NPN transistor. (8)

OR

- (b) (i) (1) Explain the avalanche effect that accounts for the reverse breakdown voltage (PIV) of a diode. (4)
- (2) What is the effect on capacitance of a PN junction diode as forward and reverse bias are applied? (4)
- (ii) (1) Explain the amplifying action of a transistor. (6)
- (2) In a CE, I_B changes from $100 \mu\text{A}$ to $150 \mu\text{A}$ which causes a change in I_C from 5 mA to 7.5 mA . If V_{CE} is held constant at 10 V , find β_{ac} (h_{fe}). (2)

14. (a) Write short notes on : (16)

- (i) RS flip-flop
- (ii) D flip-flop
- (iii) JK flip-flop
- (iv) T flip-flop

OR

(b) With necessary diagrams, explain the functioning of any one type of ADC and DAC. (16)

15. (a) Why modulation is necessary? Write in detail about frequency modulation.

OR

(b) Discuss the usage of satellite for long distance communication with a neat block diagram of basic satellite transponder.