

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 11358

B.E./B.Tech. DEGREE EXAMINATION, MAY/JUNE 2012.

Fourth Semester

Electronics and Communication Engineering

EC 1251 A — ELECTRONIC CIRCUITS – II

(Regulation 2008)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. Define ripple factor.
2. List two advantages of switched Mode Power Supply.
3. Define Barkhausen Criterion.
4. Calculate the frequency of oscillation for the clapp oscillator with $C_1 = 0.1 \mu F$, $C_2 = 1 \mu F$, $C_3 = 100 pF$ and $L = 470 \mu H$.
5. A tuned amplifier has its maximum gain at a frequency of 2MHZ and has a bandwidth of 50KHZ. Calculate the Q factor.
6. Brief the relation between bandwidth and Q factor.
7. Design an integrator to integrate a square wave of 1 MHZ.
8. Give the circuit of a diode clamper.
9. Mention any two applications blocking oscillator.
10. Define sweep time and fly back time.

PART B — (5 × 16 = 80 marks)

11. (a) Explain the action of full-wave rectifier with resistive load and give waveforms of input and output voltages. Also show that a full-wave rectifier is twice as efficient as a half-wave rectifier. (16)

Or

- (b) (i) Explain LC and CLC filters used in power supplies. (8)
(ii) Design a Zener voltage regulator to meet the following specifications: Output voltage = 5V, load current = 10mA, Zener wattage = 400mw and Input voltage = $10V \pm 2V$. (8)
12. (a) (i) Explain Wien's bridge oscillator and derive its frequency of oscillations. (10)
(ii) In Colpitt's oscillator $C_1 = 0.2 \mu F$ and $C_2 = 0.02 \mu F$. If the frequency of oscillation is 10 KHZ, find the value of the inductor. Also find the value of the inductor if C_1 is doubled. (6)

Or

- (b) (i) With neat circuit diagram, Obtain an expression for the frequency of oscillation of a Hartley oscillator. (8)
(ii) Write a note on Quartz crystal oscillators. (8)
13. (a) Sketch and explain class 'C' tuned amplifier and derive its efficiency. (16)

Or

- (b) (i) With the response characteristics explain a single-tuned amplifier. (8)
(ii) Explain Hazeltine Neutralization method. (8)
14. (a) (i) Sketch and define transistor switching times. (8)
(ii) Explain about positive, negative and combination clippers. (8)

Or

- (b) Explain the working of bi-stable multivibrators. Also brief about various triggering methods suitable for bi-stable multivibrators. (16)
15. (a) With neat circuit diagram and suitable waveforms explain Astable blocking oscillator with base timing. (16)

Or

- (b) Write short notes on:
(i) Voltage time base circuits. (8)
(ii) Current time base circuits. (8)