

PART B — (5 × 16 = 80 marks)

11. (a) (i) Given $Y(A, B, C, D) = \prod M(0, 1, 3, 5, 6, 7, 10, 14, 15)$, draw the K map and obtain the simplified expression. Realize the minimum expression using basic gates. (8)
- (ii) Implement the expression $Y(A, B, C) = \prod M(0, 2, 4, 5, 6)$ using only NOR- NOR logic. (4)
- (iii) Implement EXOR gate using only NAND gates. (4)

Or


- (b) Simplify the following function using Tabulation method $Y(A, B, C, D) = \sum m(0, 1, 2, 5, 6, 7, 8, 9, 10, 14)$ and implement using only NAND gates. (16)

12. (a) (i) Design a 3 : 8 decoder using basic gates. (8)
- (ii) Design a binary to gray code convertor. (8)

Or

- (b) (i) Design a full subtractor using demultiplexer. (8)
- (ii) Explain the working of carry-look ahead adder. (8)

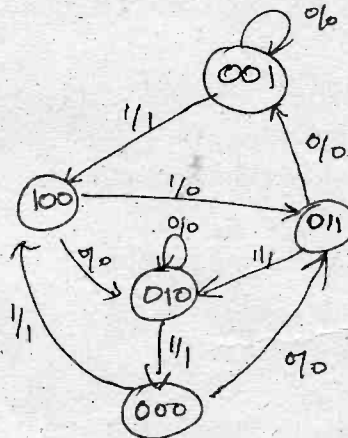13. (a) Design a sequential circuit that has 3 flip-flops A, B and C, one input x and one output y. The circuit is to be designed by treating the unused states as don't care conditions. Use JK flip-flops in the design. State diagram of the circuit is as given below. (16)



Or

- (b) Design a Moore type sequence detector to detect a serial input sequence of 101. (16)

14. (a) (i) Explain the read cycle and write cycle timing parameters of a RAM with the help of timing diagram. (8)
- (ii) Draw the Dynamic RAM cell and explain its operation. (8)

Or

- (b) Design a BCD to Excess 3 code convertor using a PLA. (16)

15. (a) Design a T flip-flop using logic gates. Derive the state table, state diagram, primitive flow table and transition table and Merger graph. Draw the logic circuit. (16)

Or

- (b) Design a asynchronous sequential circuit that has 2 input's x_1 and x_2 and one output z . When $x_1 = 0$, output is 0. The change in x_2 that occurs while x_1 is 1 will cause output $z = 1$. The output z will remain 1 until x_1 returns to 0. (16)
-