

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 51407

B.E./B.Tech. DEGREE EXAMINATION, MAY/JUNE 2014.

Fifth Semester

Electronics and Communication Engineering

EC 2305/EC 55 — TRANSMISSION LINES AND WAVEGUIDES

(Regulation 2008)

(Common to PTEC 2305 — Transmission Lines and Waveguides for B.E. (Part-Time)
Fourth Semester Electronics and Communication Engineering — Regulation 2009)

Time : Three hours

Maximum : 100 marks

(Smith chart is to be provided)

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. Write any two advantages of m-derived filters over constant-K filters.
2. Determine the value of L required by a constant-K T-section high pass filter with a cutoff frequency of 1.5 KHz and design impedance of 500Ω .
3. A transmission line has a characteristic impedance of 600Ω . Determine the magnitude of the reflection coefficient if the receiving end impedance is $(650 - j 475)\Omega$.
4. Define insertion loss.
5. Give the equations for the characteristic impedance and propagation constant of a dissipationless line.
6. Mention the disadvantages of single stub matching.
7. A wave is propagated in the dominant mode in a parallel plane waveguide. The frequency is 6 GHz and the plane separation is 4 cm. Calculate the cutoff wavelength and the wavelength in the waveguide.
8. Give the equations for the propagation constant and wavelength for TEM waves between parallel planes.
9. What are the advantages and applications of cylindrical waveguides?
10. Mention the different types of guide termination.

PART B — (5 × 16 = 80 marks)

11. (a) (i) Draw and explain the design and operation of m-derived T-section bandpass filter with necessary equations and diagrams. (8)
- (ii) Design constant-K bandstop filters (both T and π -sections) for the cutoff frequencies of 2 KHz and 6KHz. The design impedance is 500 Ω . (8)

Or

- (b) (i) Explain the principle and operation of crystal filters with neat diagrams. (10)
- (ii) Design an m-derived low pass filter with a cutoff frequency of 2 KHz. Design impedance is 500 Ω and $m = 0.4$. Consider a π -section for your calculation. (6)
12. (a) (i) What are the types of waveform distortion introduced by a transmission line? Derive the conditions for the distortionless operation of a transmission line. (10)
- (ii) The constants of a transmission line are $R = 6 \Omega/\text{km}$, $L = 2.2 \text{ mH}/\text{km}$, $C = 0.005 \mu\text{F}/\text{km}$ and $G = 0.25 \times 10^{-3} \text{ mhos}/\text{km}$. Calculate the attenuation constant (α) and phase constant (β) at 1000 Hz. (6)

Or

- (b) (i) Derive the transmission line equations and obtain expressions for the voltage and current on a transmission line. (10)
- (ii) A transmission line has a characteristic impedance of $(683 - j138)\Omega$. The propagation constant is $(0.0074 + j 0.0356)$ per km. Determine the values of R and L of this line if the frequency is 1000 Hz. (6)
13. (a) (i) Derive an expression for the input impedance of a dissipationless line. Extend your results for open and short circuited lines also. (10)
- (ii) Write a brief note on impedance measurement on transmission lines. (6)

Or

- (b) (i) Discuss the principle of double stub matching with neat diagram and expressions. (8)
- (ii) A single stub is to match a 300Ω line to a load of $(180 + j120)\Omega$. The wavelength is 2 meters. Determine the shortest distance from the load to the stub location and proper length of the short circuited stub using relevant formula. (8)

14. (a) Discuss the transmission of TM waves between parallel perfectly conducting planes with necessary expressions for the field components. Discuss the characteristics of TE and TM waves between the parallel planes. (16)

Or

- (b) (i) Discuss briefly the attenuation of TE and TM waves between parallel planes. (8)
- (ii) Describe the manner of wave travel between parallel planes with necessary expressions for their velocities. (8)
15. (a) (i) Describe the propagation of TE waves in a rectangular waveguide with necessary expressions for the field components. (10)
- (ii) An air filled rectangular waveguide of dimensions $a = 6$ cm and $b = 4$ cm operates in the TM_{11} mode. Find the cutoff frequency, guide wavelength and phase velocity at a frequency of 3 GHz. (6)

Or

- (b) (i) Describe the principle and operation of rectangular cavity resonators with relevant expressions. (10)
- (ii) Give a brief note on excitation of modes in rectangular waveguides. (6)