





## PART - B

(5×16=80 Marks)

11. a) Determine the stability factor due to change in  $h_{fe}$  and  $V_{BE}$  of voltage divider bias circuit. (16)

(OR)

- b) The device parameters for the circuit configuration given in Figure-1 are  $h_{fe} = 100$  and  $V_{BE(on)} = 0.7V$ . The circuit is to be biased with  $V_{CC} = +10V$  and transistor quiescent values should be  $I_{CQ} = 1\text{ mA}$  and  $V_{CEQ} = 5V$ . Calculate  $I_{CQ}$ ,  $V_{CEQ}$  for  $h_{fe} = 50, 100, 150$  and  $200$  and comment on the results. (16)

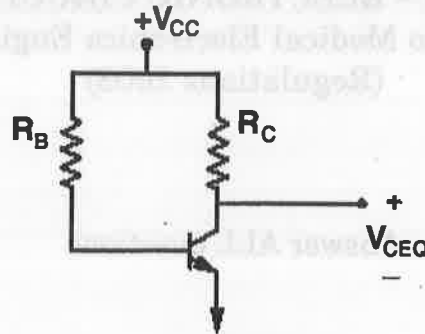


Figure-1

12. a) Determine the voltage gain and current gain of a darlington pair (BJT) amplifier. (16)

(OR)

- b) Determine the voltage gain, input impedance and output impedance of Common-Gate (FET) amplifier. (16)

13. a) Determine the upper cut-off frequency of CE amplifier using miller approximation method. (16)

(OR)

- b) For the circuit shown in Figure-2, the NFET transistor parameters are :  $g_m = 2\text{ mA/V}$ ,  $I_{DQ} = 4\text{ mA}$  and  $V_A = 100V$ ,  $C_{gs} = 1\text{ pF}$  and  $C_{gd} = 0.4\text{ pF}$ . The amplifier has  $R_G = 100\text{ k}\Omega$ ,  $R_D = R_L = 15\text{ k}\Omega$ . Calculate the mid-band gain, upper cut-off frequency. Also find the values of  $C_G$ ,  $C_D$  and  $C_S$  by assuming lower cutoff frequency of  $100\text{ Hz}$  and that the nearest break frequency be atleast a decade lower. (16)

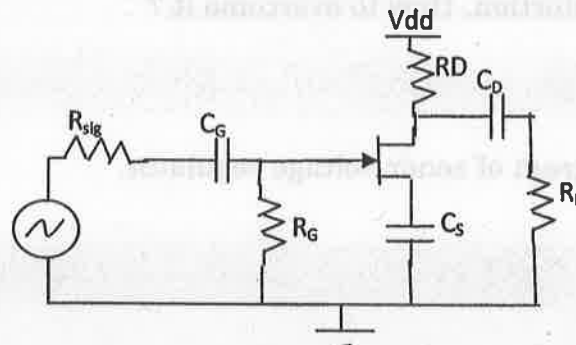


Figure-2



14. a) Determine the maximum power dissipation in a transistor (with and without heat sink). Consider the power device for which the thermal resistance parameters are :

$$\theta_{\text{dev-case}} = 1.75^{\circ}\text{C/W}, \theta_{\text{case-sink}} = 1.0^{\circ}\text{C/W}, \theta_{\text{sink-amb}} = 5^{\circ}\text{C/W} \text{ and } \theta_{\text{case-amb}} = 50^{\circ}\text{C/W}.$$

The ambient temperature is  $T_{\text{amb}} = 30^{\circ}\text{C}$  and the maximum junction or device temperature  $T_{\text{jma}} = T_{\text{dev}} = 150^{\circ}\text{C}$ . Comment on the results. (16)

(OR)

- b) Determine the maximum conversion efficiency of Class-A power amplifier. (16)

15. a) Explain the Half-wave rectifier in terms of average value of output voltage and current, Ripple factor and Rectification efficiency. (16)

(OR)

- b) Explain how the output voltage is controlled by zener voltage regulator during varying input voltage and variable load resistance. (16)

