



Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : X20480

B.E./B.Tech. DEGREE EXAMINATIONS, APRIL/MAY 2021

Third Semester

Electrical and Electronics Engineering

EE 6303 – LINEAR INTEGRATED CIRCUITS AND APPLICATIONS

(Common to Electronics and Instrumentation Engineering and Instrumentation and Control Engineering)

(Regulations 2013)

(Common to PTEE6303 – Linear Integrated Circuits and Applications for B.E.

(Part-Time)/Third Semester Electronics and Electronics Engineering – Regulations 2014)

Time : Three Hours


Maximum : 100 Marks

Answer ALL questions

PART – A

(10×2=20 Marks)

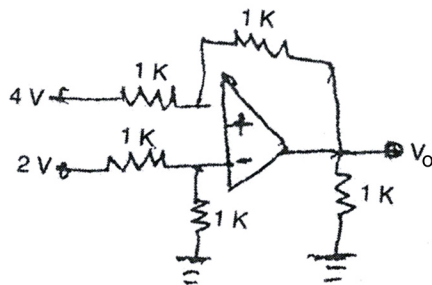1. State the limitations of IC technology.
2. Distinguish between dry etching and wet etching.
3. Draw the circuit diagram of a symmetrical emitter coupled differential amplifier.
4. For the circuit diagram shown below determine the output voltage V_o .



5. Draw the circuit of a log amplifier using two op-amps.
6. Calculate the value of the LSB, MSB and full scale output for an 8-bit DAC for the 0 to 12 V range.
7. Draw the functional block of 555 timer IC.
8. Define PLL.
9. What are the limitations of three terminal regulator ?
10. How current boosting is achieved in a 723 IC ?

**PART – B****(5×13=65 Marks)**

11. a) i) Distinguish diffusion and ion implantation process in IC fabrication. (5)
ii) Describe the metallization process, assembly processing and packaging with neat diagram. (8)
(OR)
- b) Discuss briefly about the PN junction diode and JFET fabrication.
12. a) Discuss in detail about the DC and AC characteristics of op-amp. (13)
(OR)
- b) Explain the differential amplifier using op-amp. (13)
13. a) i) Discuss the second order high pass filter with its frequency response and design the circuit with the cut-off frequency of 5 KHz. (7)
ii) With a neat circuit diagram, explain the working of Schmitt trigger using op-amp. (6)
(OR)
- b) i) Explain the working of instrumentation amplifier. (7)
ii) With neat circuit diagram, explain the operation of R-2R D/A converter. (6)
14. a) i) Draw and explain the functional diagram of 555 timer. (8)
ii) Discuss the operation of a FSK generator using 555 timer. (5)
(OR)
- b) Draw the block diagram of a VCO and explain its operation.
15. a) With necessary diagram and waveforms explain the working principle of switched mode power supply. (13)
(OR)
- b) Write short notes on the following :
i) LM 380 power amplifier. (6)
ii) ICL 8038 function generator. (7)

PART – C**(1×15=15 Marks)**

16. a) Sketch the implementation of an instrumentation amplifier using three op-amps. Explain the principle of operation and its applications. (15)
(OR)
- b) Using 7805 design a current source to deliver a 0.2A current to a 22 ohm 10 w load. (15)
-