

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code : 20408**

B.E./B.Tech. DEGREE EXAMINATION, NOVEMBER/DECEMBER 2018.

Third Semester

Electronics and Communication Engineering

EC 6302 — DIGITAL ELECTRONICS

(Common to Mechatronics Engineering, Robotics and Automation Engineering)

(Regulations 2013)

(Also common to PTEC 6302 — Digital Electronics for B.E. (Part-time) Second Semester — Electronics and Communication Engineering — Regulations 2014)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. What are the universal gates? Justify.
2. State De-Morgan's Theorem.
3. Write the characteristic equation of  $4 \times 1$  Multiplexer.
4. State the differences between combinational and sequential circuits.
5. Draw the excitation table for D Flip Flop.
6. Draw the state diagram of 3 bit up counter.
7. Compare PAL, PLA and PROM.
8. Define setup-time with timing diagram.
9. Mention the types of sequential circuits and give the difference between them.
10. Define Mealy machine with a state diagram.

PART B — (5 × 13 = 65 marks)

11. (a) Simplify  $f(W, X, Y, Z) = \sum m(2, 6, 8, 9, 10, 11, 14, 15)$  using Quine – Mc Cluskey method of minimization.

Or

- (b) Draw and Explain NAND, NOT and NOR gate CMOS representation.

12. (a) Draw  $4 \times 1$  multiplexer and  $1 \times 4$  Demultiplexer using gates and explain its operation.

Or

- (b) Design a 2 bit magnitude comparator and draw its logic circuit.

13. (a) Explain the logic circuit, characteristic and excitation table of JK, SR and D flip flop.

Or

- (b) Design a 3 bit synchronous binary up-down binary using T flip flop.

14. (a) Design and implement a BCD to gray code converter using PAL.

Or

- (b) Write short notes on Static, Bipolar and MOSFET RAM cell.

15. (a) Elucidate the design procedure of synchronous sequential circuits.

Or

- (b) Design a sequential circuit whose state tables are specified in the Table below using D flip-flops.

Present State Q <sub>0</sub> Q <sub>1</sub>	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
00	00	01	0	0
01	00	10	0	0
10	11	10	0	0
11	00	01	0	1


PART C — (1 × 15 = 15 marks)

16. (a) (i) Design a circuit that has a 3-bit binary input and a single output (Z) specified as follows : (8)

$Z = 0$ , when the input is less than  $5_{10}$

$Z = 1$ , otherwise

 - (ii) Simplify the given logic circuit using Boolean Simplification. (7)



Or

- (b) Design a synchronous sequential circuit whose state diagram is shown below. (15)

