

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code : 20471**

B.E./B.Tech. DEGREE EXAMINATIONS, APRIL/MAY 2022.

Fourth Semester

Electronics and Communication Engineering

EC 8452 – ELECTRONIC CIRCUITS – II

(Common to: Electronics and Telecommunication Engineering)

(Regulations 2017)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. Define sensitivity and de-sensitivity of gain in feedback amplifiers.
2. Write the expression for input and output resistance of voltage series feedback amplifier.
3. If  $L_1=2$  mH,  $L_2=4$  mH and  $C=0.1$  nF, Observe the frequency of oscillation for Hartley oscillator.
4. In an RC phase shift oscillator, if  $R_1 = R_2 = R_3 = 200k\Omega$  and  $C_1 = C_2 = C_3 = 100$  pF. Detect the frequency of oscillations.
5. Illustrate the applications of tuned amplifiers.
6. Define unloaded and loaded Q of tank circuits.
7. Identify how the high pass RC circuit acts as a differentiator.
8. Compare Astable, Monostable and Bistable multivibrators.
9. Give the principle of operation of step-down DC-DC converter.
10. Compare Buck and Boost converter.

PART B — (5 × 13 = 65 marks)

11. (a) Draw the block diagram of Voltage series feedback amplifiers and derive the expressions of input impedance  $R_{if}$ , output impedance  $R_{of}$  and gain.

Or

- (b) Build the circuit diagram of current shunt feedback amplifier and develop the expressions for  $R_{if}$  and  $R_{of}$ .
12. (a) Demonstrate the working principle of RC phase shift oscillator circuit diagram also derive the expression for frequency of oscillation and condition for sustained oscillation.

Or

- (b) Estimate the frequency of oscillation and the condition for sustained oscillation of Colpitts oscillator with neat circuit diagram.
13. (a) Demonstrate a capacitance coupled single tuned amplifier circuit and derive the expressions for its important parameters.

Or

- (b) Conclude the following with neat circuit diagram:
- (i) Hazeltine neutralization
  - (ii) Neutrodyne neutralization
14. (a) (i) Classify the various types of diode clippers (5)
- (ii) Demonstrate the diode clippers with appropriate diagrams and waveforms. (8)

Or

- (b) Illustrate the operation of collector coupled Astable multivibrator with neat diagrams and waveforms. (13)
15. (a) Summarize the transfer characteristic, signal waveforms, power dissipation, power conversion efficiency of Class A amplifier.

Or

- (b) Illustrate the Buck converter with necessary diagrams and derive the expressions for voltage and current.

PART C — (1 × 15 = 15 marks)

16. (a) Explain the gain of Wein bridge oscillator using BJT amplifier with necessary equations and diagrams.

Or

- (b) In a Colpitts oscillator, the values of the inductors and capacitors in the tank circuit are  $L = 40\text{mH}$ ,  $C_1 = 100\text{pF}$  and  $C_2 = 500\text{pF}$ . Evaluating the following (15)

- (i) Frequency of oscillations.
- (ii) If the output voltage is  $10\text{v}$ , find the feedback voltage.
- (iii) Find the minimum gains if the frequency is changed by changing  $L$  alone.
- (iv) Find the value of  $C_1$  for a gain of 10.
- (v) Also find the new frequency.

