

Reg. No. :

Question Paper Code : 70513

B.E./B.Tech. DEGREE EXAMINATIONS, NOVEMBER/DECEMBER 2023.

Fourth Semester

Electronics and Communication Engineering

EC 8452 — ELECTRONIC CIRCUITS – II

(Common to: Electronics and Telecommunication Engineering)

(Regulations 2017)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. How does negative feedback affect the stability of an amplifier circuit?
2. A feedback amplifier has an open loop gain of 500 and a feedback factor of $\beta = 0.02$. Find the closed loop gain of the circuit when a negative feedback is introduced.
3. Why are RC oscillators preferred for the generation of low frequencies?
4. Draw the circuit of a Hartley oscillator.
5. Define Q factor.
6. Determine the bandwidth of a 3 stage cascaded single tuned amplifier if its resonant frequency is 400 KHZ and the loaded Q of each stage is 10.
7. Write the output equation and draw the output waveform of the given circuit (Figure. 7) if the input is $V_i = V_m \sin \omega t$.

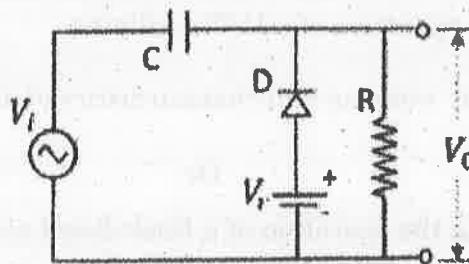


Figure. 7

8. Give two applications of Schmitt trigger.
9. Differentiate power amplifiers from voltage amplifiers.
10. Distinguish between class A, class B, and Class C amplifiers.

PART B — (5 × 13 = 65 marks)

11. (a) Discuss of the effect of negative feedback on the frequency response of an amplifier with necessary diagrams and derivations.

Or

- (b) Derive the expression for gain, input resistance and output resistance of a voltage series and a current shunt feedback amplifiers.

12. (a) Derive the transfer functional a phase lead-lag network and hence obtain the frequency of oscillation of a Wein bridge oscillator.

Or

- (b) (i) A quartz crystal has $L = 3 \text{ H}$, $C = 0.01 \text{ pF}$ and $R = 2\text{K}\Omega$. Its mounting capacitance is 2 pF . Calculate its series and parallel resonance. (8)

- (ii) How is amplitude stabilization achieved in an oscillator circuit? (5)

13. (a) What is a stagger tuned amplifier? Explain its operation.

Or

- (b) What is neutralization? Why is it required in tuned amplifiers? Explain Hazeltine neutralization technique with neat diagram.

14. (a) What is a multivibrator? How is it different from an oscillator? Explain the operation an astable multivibrator.

Or

- (b) Explain the operation of a UJT oscillator.

15. (a) Illustrate the working and characteristics of a power MOSFET.

Or

- (b) Demonstrate the operation of a Busk-Boost converter.

PART C — (1 × 15 = 15 marks)

16. (a) Analyze the given circuit (Figure. 16(a)) and find its voltage gain, input and output resistance if its transistor parameters are $h_{ie} = 1k$, $h_{fe} = 100$, $h_{re} = 0$.

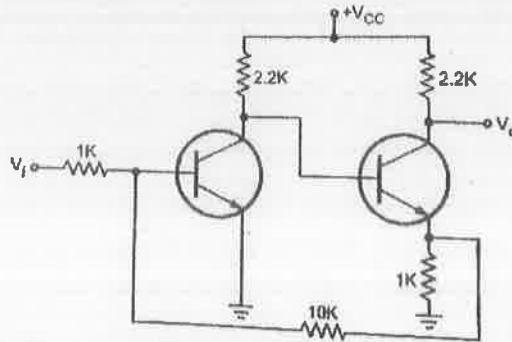


Figure. 16(a)

Or

- (b) Design a single tuned amplifier, to have a center frequency of 500 KHz and a bandwidth of 10 KHz. The transistor parameters are $g_m = 0.04 S$, $h_{fe} = 100$, $C_{be} = 1000 pF$, $C_{bc} = 100 pF$. The bias network and the input resistance are adjusted so that $r_i = 4K \Omega$, and $R_L = 100 \Omega$.