



Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 91480

B.E./B.Tech. DEGREE EXAMINATIONS, NOVEMBER/DECEMBER 2019

Third Semester

Electrical and Electronics Engineering

EE 6301 – DIGITAL LOGIC CIRCUITS

(Common to Electronics and Instrumentation Engineering, Instrumentation and Control Engineering)

(Regulations 2013)

(Also common to PTEE 6301 – Digital Logic Circuits for B.E.(Part-Time) – Third Semester – Electrical and Electronics Engineering – Regulations 2014)

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions

PART – A

(10×2=20 Marks)

1. Reduce $a(b + bc') + ab'$.
2. Convert 143_{10} into its binary and binary coded decimal equivalent.
3. Convert the given expression in canonical SOP form
 $Y = AC + AB + BC$.
4. Simplify the expression $Z = AB + A\bar{B} \cdot (\bar{A}\bar{C})$.
5. Give the characteristic equation and characteristic table of SR flip-flop.
6. State any two differences between Moore and Mealy state machines.
7. What happens to the information stored in a memory location after it has been read and write operation ?



8. What is Programmable Logic Array ?
9. Write VHDL behavioral model for D flip-flop.
10. Write the VHDL code for a logical gate which gives high output only when both the inputs are high.

PART – B

(5×13=65 Marks)

11. a) i) Convert 1010111011101100_2 into its octal, decimal and hexadecimal equivalent. (6)
ii) Deduce the odd parity hamming code for the data : 1010.
Introduce an error in the LSB of the hamming code and deduce the steps to detect the error. (7)
(OR)
- b) i) With circuit schematic explain the operation of a two input TTL NAND gate. (6)
ii) With circuit schematic and explain the operation and characteristics of a ECL gate. (7)
12. a) Simplify the logical expression using K-map in SOP and POS form
 $F(A, B, C, D) = \sum m(0, 2, 3, 6, 7) + d(8, 10, 11, 15)$. (13)
(OR)
- b) Design a full subtractor and realise using logic gates. Also, implement the same using half subtractors. (13)
13. a) i) Explain the operation of a master slave JK flip-flop. (7)
ii) Design a 3-bit bidirectional shift register. (6)
(OR)
- b) i) Design a MOD-5 synchronous counter using JK flip-flops. (7)
ii) Design a sequence detector to detect the sequence 101 using JK flip-flop. (6)
14. a) Design an asynchronous sequential circuit that has two inputs X_2 and X_1 and one output Z. When $X_1 = 0$, the output Z is 0. The first change in X_2 that occurs while X_1 is 1 will cause output Z to be 1. The output Z will remain 1 until X_1 returns to 0.
(OR)



- b) i) Implement the following function using PLA : (7)
 $F(x, y, z) = \Sigma m(1, 2, 4, 6)$
- ii) For the given Boolean function, obtain the hazard-free circuit. (6)
 $F(A, B, C, D) = \Sigma m(1, 3, 6, 7, 13, 15).$
- 15. a) Write a VHDL code to realize a full adder using behavioural modeling and structural modeling. (13)
(OR)
- b) i) Discuss briefly the packages in VHDL. (6)
- ii) Write an VHDL coding for realization of clocked SR flip-flop. (7)

PART – C

(1×15=15 Marks)

- 16. a) i) A sequential circuit with D flip-flops A and B, input X and Y is specified by the following next state and output equations,
 $A(t + 1) = AX + BX,$
 $B(t + 1) = \overline{AX}$
 $Y = (A + B)\overline{X}$
Draw the logic diagram, derive state table and state diagram. (12)
 - ii) Realize T flip-flop using JK flip-flop. (3)
(OR)
 - b) i) Design a full Adder using 4×1 multiplexer, also write its truth table and draw the logical diagram. (10)
 - ii) Describe level triggering and edge triggering. (5)
-

