



ST. ANNE'S

COLLEGE OF ENGINEERING AND TECHNOLOGY
(Approved by AICTE, New Delhi. Affiliated to Anna University, Chennai)
(An ISO 9001: 2015 Certified Institution)
ANGUCHETTYPALAYAM, PANRUTI – 607 106.

QUESTION BANK

PERIOD: JULY - NOV 2018

BATCH: 2017 – 2021

BRANCH: ECE

YEAR/SEM: II/III


SUB CODE/NAME: EC8351 – ELECTRONIC CIRCUITS 1

UNIT I

BIASING OF DISCRETE BJT, JFET AND MOSFET


PART A

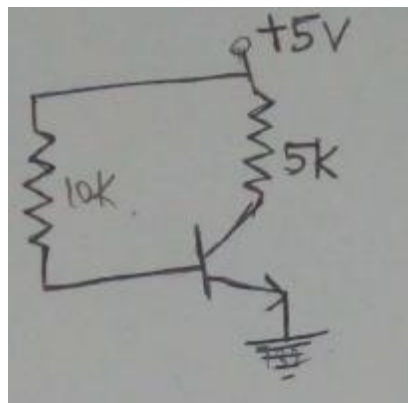1. What is diode compensation? [D] (April/May 2018)
2. Sketch the fixed bias circuit of the JFET? [D] (April/May 2018)
3. What is the thermal runaway? [D] (Nov/Dec 2017)
4. List out three stability factors. [D] (April/May 2017)
5. Find the collector and base current of circuit given in below fig $h_{fe} = 80$, $V_{be(ON)} = 0.7V$ [ID] (April/May 2017)



6. What is a Q point? [ID] (Nov/Dec 2016)
7. What is the impact of temperature on drain current of MOSFET? [ID] (Nov/Dec 2016)
8. What is an operating point? [D] (May/June 2016, Nov/Dec 2017)
9. Give the methods of biasing a JFET? [D] (May/June 2016)
10. List out the importance of selecting the proper operating point? [ID] (April/May 2015)
11. Define stability factor w.r.t β , V_{be} , I_{co} [D] (Nov/Dec 2009, Nov/Dec 2015)
12. What is the need of a load line [D] (Nov/Dec 2016)
13. Define AC load line. [D] (Nov/Dec 2016)
14. Write the types of FET biasing. [D] (May/June 2016)
15. What are the parameters that affect the stability [ID] (May/June 2014)
16. Draw the DC load line of the circuit shown in Figure. [ID] (April/May 2015)

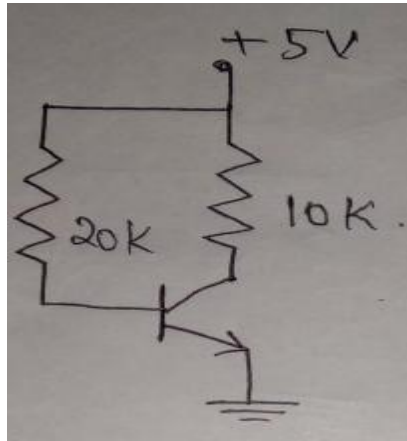17. Find the collector and base current of circuit given in below fig $h_{fe} = 100$, $V_{be(ON)} = 0.7V$ [ID]
(Nov/Dec 2014)




18. What are the operating regions of N-channel MOSFET and how do you identify the operating region? [ID] (Nov/Dec 2014)
19. Derive for the stability factor S for a fixed bias circuit. [ID] (Nov/Dec 2010)
20. Draw the circuit of self-bias using BJT. [D] (May/June 2011)
21. Write the conditions of thermal stability. [D]
22. Write the application of JFET. [D]
23. Write the general expression for stability factor. [ID]
24. What is the advantage of using emitter resistance in the context of biasing? [ID]
25. What is the impact of temperature on drain current of MOSFET? [ID]
26. What are the advantage and disadvantage of fixed bias. [D]
27. What is bias compensation using thermistor? [D]
28. Why is temperature compensation is required? [ID]
29. List out the various biasing circuits in BJT? [D]
30. Differentiate bias stabilization and compensation techniques. [D]

PART B


[FIRST HALF]

BJT– Need for biasing - DC Load Line and Bias Point – DC analysis of Transistor circuits

 
1. Briefly explain the reason for keeping the operating point of a transistor as fixed. [ID] (7) (April/May 2017)
2. Consider the circuit shown below with transistor parameters $I_{DSS} = 12 \text{ mA}$, $V_P = -4V$, and $\lambda = 0.008 \text{ V}^{-1}$. Determine the small signal voltage gain $A_v = V_o/V_i$. [ID] (13) (Nov/Dec 2016)
3. The parameters for each transistor in the circuit in below figure are $h_{fe} = 100$ and $V_{BEon} = 0.7V$. Determine the Q point values of base, collector and emitter currents in Q_1 and Q_2 [ID]. (7) (April/May 2015)



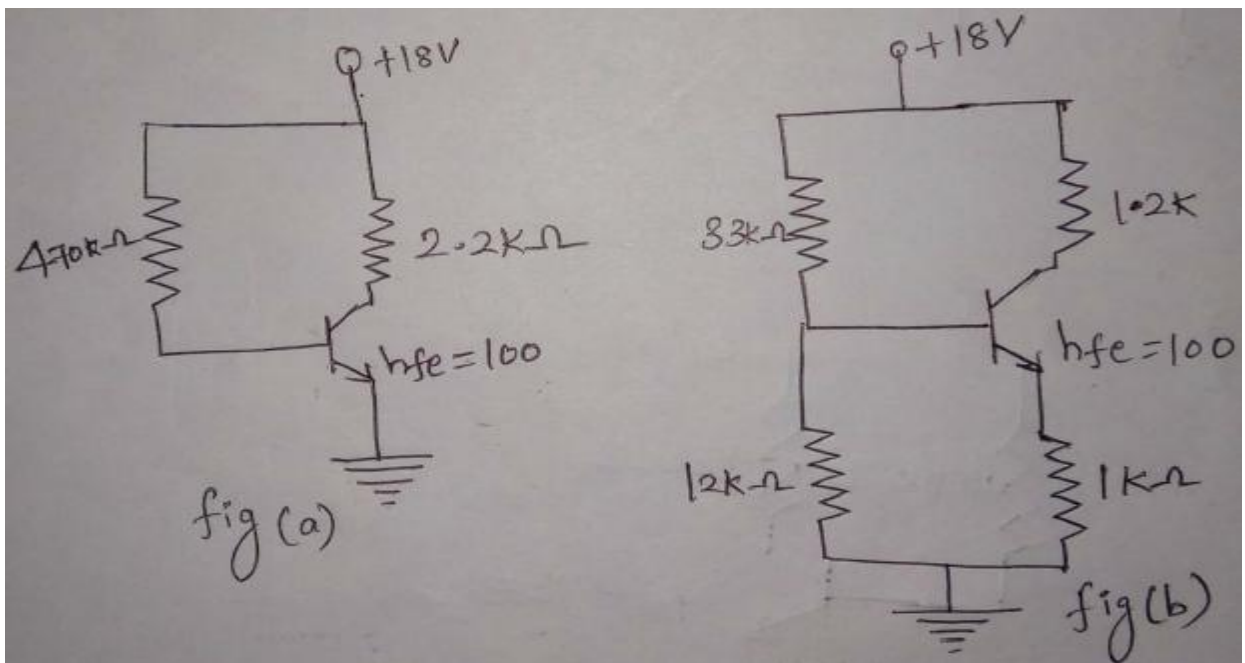4. Determine the change in collector current produced in each bins referred to in figures (a) and (b), when the circuit temperature raised from 25°C to 105°C and $I_{CBO} = 15 \text{ Na}$ @ 25°C. [ID] (7) (April/May 2015)



 5. Design Emitter bias for BJT with $I_c = 2\text{mA}$, $V_{cc} = 18\text{V}$, $V_{ce} = 10\text{V}$ and $\beta = 150$. [ID] (7) (N/D 14)
6. The circuit in below figure let $h_{fe} = 100$. Find V_{TH} and R_{TH} for the base circuit. Determine I_{CQ} and V_{CEQ} . Draw the DC load line. (7) [D] (April/May 2015)



Various biasing methods of BJT – Bias Circuit Design -

7. Compare the various methods of biasing using BJT in terms of their stability factors. **(13) [D] (May/June 2016)**
8. Explain about the voltage divider bias of BJT and derive the expression for stability factor. **(13) [D] (April/May 2018, Nov/Dec 2017, Nov/Dec 2015)**
9. Derive the stability Factors for voltage divider bias circuit and give reason why it is advantageous than fixed bias circuit. **(13) [D] (April/May 2017)**
10. Explain the fixed bias of BJT & derive the expression for stability factor **(13) [D] (May/June 2015)**
11. With a neat diagram explain the voltage divider biasing and calculate the stability factor for BJT **[D] (15) (April/May 2018, Nov/Dec 2017, Nov/Dec 2015)**

Stability factors

12. Derive the stability factor of Self bias circuit of BJT **(6) [D] (Nov/Dec 2014)**
13. Draw a self (Voltage divider bias) bias and derive the all stability factors S, S', S'' . **(D)**

[SECOND HALF]

Bias compensation techniques using Diode


14. Draw a circuit which uses a diode to compensate for changes in I_{co} . Explain how stabilization is achieved in the circuit. **(7) [D] (April/May 2017)**
15. With neat diagram explain two bias compensation techniques and state its advantages and disadvantages. **(13) [D] (May/June 2016)**

JFET - DC Load Line and Bias Point - JFET Bias Circuit Design

16. Determine the quiescent current and voltage values in a p-channel JFET circuit. **(6) [D] (April/May 2015)**
17. What is the need for biasing, Define DC & AC load line? How JFET acts as a VVR **[ID] (Nov/Dec 2015)**

MOSFET Biasing - Biasing FET Switching Circuits.

 
18. With a neat diagram explain the source and drain resistance biasing of MOSFET. **(13) [D] (N/D'17)**
19. Design voltage divider bias circuit for NMOS, such that $I_{DQ} = 400 \mu\text{A}$, $V_{DD} = 14\text{V}$, $V_{DS} = 2.3\text{V}$, $k_n = \mu_n C_{ox}(W/L) = 1\text{mA}/\text{V}^2$, $V_t = 1\text{V}$. Assume a current of $1\mu\text{A}$ through R_1 and R_2 , and $V_s = 1.2\text{V}$ **(13) [ID] (April/may 2015)**



20. Analyze a BJT with a voltage divider bias circuit, and determine the change in the Q-Point with a variation in β when the circuit contains an emitter resistor. Let the biasing resistors be $R_{B1} = 56K\Omega$, $R_{B2} = 12.2K\Omega$, $R_c = 2K\Omega$, $R_E = 0.4K\Omega$, $V_{cc} = 10V$, $V_{BE(on)} = 0.7V$, and $\beta = 100$. (15) [D] (Nov/Dec 2016)

UNIT- II
BJT AMPLIFIERS
PART A

 1. Why CE configuration is preferred for Amplification? [ID] (Apr/May 2018)
2. What is bypass and coupling capacitor? [D] (Nov/Dec 2017)
3. List the need for bootstrapping in amplifier? [ID] (Nov/Dec 2017)
4. Define millers theorem [D] (May/June 2010, Nov/Dec2015, April/May 2017)
5. Draw the small signal ac equivalent circuit of the BJT. [D] (Nov/Dec 2016, April/May 2017)
6. What is an ac load line. [D] (Nov/Dec 2016)
7. What is the need of load line. [ID] (May/June 2016)
8. Draw a cascade amplifier and its ac equivalent circuit. [D] (May/June 2016, April/May 18)
9. Define CMRR of BJT differential amplifier. How it improved? [ID] (Apr/May 2015, Nov/Dec 2016)
10. A small signal source $V_i(t) = 20\cos 20t + 30\sin 10^6t$ is applied to a transistor to a transistor amplifier as shown in below fig. The transistor has $h_{fe} = 150$, $r_o = \infty$ and $R_{\pi} = 3K\Omega$. Determine $V_o(t)$. [ID] (Apr/May 2015)



11. Draw the hybrid model of CE amplifier [ID] (Nov/Dec 2009, Nov/Dec 2016)
12. State the various methods of improving CMRR. [ID] (Nov/Dec 2014)
13. List out the advantages of h parameters [D] (Nov/Dec 2014)
14. Find CMRR of differential amplifier with differential gain of 300 and common mode gain of 0.2. [ID] (Nov/Dec 2014)
15. Write the characteristics of CE amplifier [D] (May/June 2014)
16. Draw the hybrid model of CC amplifier. [D]
17. Draw the circuit diagram of Darlington type amplifier [D] (May/June 2013)
18. Write the characteristics of CC amplifier [D] (Nov/Dec 2013)
19. How are amplifiers classified according to the transistor configuration [ID] (Nov/Dec 2015)
20. What is Darlington Connection [D] (May/June 2014)
21. What are the Coupling schemes used in multistage amplifiers [D] (May/June 2010)
22. Draw the circuit diagram of Darlington type amplifier [D] (May/June 2013)
23. Draw a Darlington amplifier with Bootstrap Management [ID] (Nov/Dec 2010)
24. Write the characteristics of CC amplifier [D] (Nov/Dec 2013)
25. What is the advantage of Darlington amplifier [D] (Nov/Dec 2013)
26. What is the main application of CB configuration of transistor [ID]
27. What are the limitations of h-parameters [D]
28. Draw the hybrid model of CC amplifier [D]
29. What is bootstrapping. [D]
30. Why constant current source biasing is preferred for differential amplifier

PART B

[FIRST HALF]

Single stage and Multi-stage amplifier

1. Compare and contrast of single stage and Multistage amplifier. [D] (15) (April/may 2018)

Analysis of CE, CC and CB amplifiers using Hybrid π equivalent circuits

2. Derive the expressions for the voltage gain, current gain, input and output impedance of emitter follower amplifier. (13) [D] (April/May 2018)
3. Draw the a.c equivalent circuit of a CE amplifier with voltage divider bias and derive the expression for current gain, voltage gain, input impedance, output admittance and overall current gain. (13) [D] (April/May 2017)
4. Explain about CB amplifier and derive the expression for gain, R_i , R_o . (13) [D] (Nov/Dec 2016)
5. Explain about CE amplifier with emitter resistor and an emitter bypass capacitor are incorporated in the design? Explain with necessary equations. (13) [D] (Nov/Dec 2014, (May/June 2016)

6. Compare CB, CE and CC amplifiers and state their applications (7) [D] (May/June 2012)
7. Calculate the small signal voltage gain of an emitter follower circuit. Given $\beta=100, V_{BE}=0.7V, V_A=80V, I_{CQ}=0.793mA, V_{CEQ}=3.4V$. (7) [ID] (May/June 2016)
8. What are the changes in the a.c characteristics of a common emitter amplifier when an emitter resistor and an emitter bypass capacitor are incorporated in the design? Explain with necessary equations. [ID] (May/June 2016)


Darlington Amplifier - Bootstrap technique

9. Draw and explain the operation of a Darlington amplifier. (7) [D] (May/June 2016)
10. Explain the boot strapped Darlington emitter follower with circuit diagram (13) [ID] (N/D 14).
11. With neat diagrams, explain the operation and advantages of Darlington pair circuit. Also analyze its small-signal voltage gain and input impedance. (13) [ID] (Nov/Dec 2016)


[SECOND HALF]

Cascade and Cascode configurations

 12. Write short notes on multistage amplifiers. Draw a two stage RC coupled amplifier and explain. Also compare Cascade and Cascode amplifier. (13) [D] (April/May 2018)
13. (i) Explain the operation of Cascode amplifier and derive gain, input impedance and output impedance (13) [D] (Nov/Dec 2014)
14. Consider the circuit shown in fig with the parameters are $h_{fe} = 120, V_0 = \infty$. Determine the current gain, voltage gain, input impedance and output impedance. Find the maximum undistorted output voltage swing. (13) [ID] (April/May 2015)
15. Compare and contrast on the design of bandwidth of the single stage and multi stage amplifiers. (15) [D] (April/May 2018)
16. What is Cascade Amplifier? Explain with necessary equations and explain how to determine its bandwidth. (15) [D] (Nov/Dec 2017)
17. Calculate the input and output resistance of the emitter- follower circuit shown in below Fig. Assume $R_3 = 0.5 k, r_{\pi} = 3.28 K\Omega, \beta = 100$ and $R_o = 100 K\Omega$. (15) [ID] (April/May 2017)



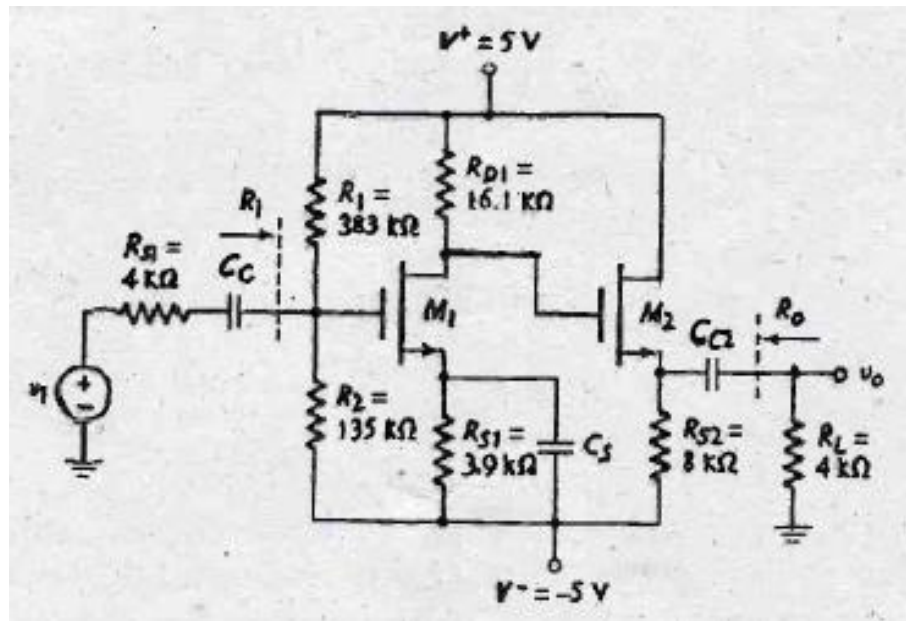18. Determine the small signal voltage gain of a multistage cascade circuit shown in the figure below. The transistor parameters are $K\alpha_1 = 0.5 \text{ mA/V}^2$, $K\alpha_2 = 0.2 \text{ mA/V}^2$, $V_{TN1} = V_{TN2} = 1.2 \text{ V}$ and $\lambda_1 = \lambda_2 = 0$. The quiescent drain currents are $I_{D1} = 0.2 \text{ mA}$ and $I_{D2} = 0.5 \text{ mA}$. (13) [D] (Nov/Dec 2016)



Differential amplifier

19. Summarize the working principle of CMOS differential amplifier with the neat diagram. Also determine its CMRR. (15) [ID] (April/May 2018, Nov/Dec 2017)
20. Explain in detail the transfer characteristics of differential amplifier. Explain the method used to improve CMRR. (16) [ID] (Nov/Dec 2015)

UNIT-III


SINGLE STAGE FET, MOSFET AMPLIFIERS

PART A

1. What is I_{DSS} in a JFET? [D] (April/May 2018)
2. Why MOSFETs are used? [ID] (April/May 2018)
3. What is BiMOS? [ID] (May/June 2016) (Nov/Dec 2017)
4. A self biased P -channel JFET has a pinch off voltage of 5V and $I_{DSS} = 12 \text{ mA}$. The supply voltage is 12 V. Determine the value of resistors R_D and R_S , so that $I_D = 5 \text{ mA}$ and $V_{DS} = 6 \text{ V}$. [ID] (Nov/Dec 2017)
5. What are the features of BiMOS cascode amplifier. [ID] (April/May 2017, N/D 2014)
6. What is the use of source bypass capacitor in CS amplifier. [ID] (April/May 2017)
7. What is the impact of including a source resistor in the FET amplifier [ID] (Nov/Dec 2016)
8. Why multistage amplifiers is required? [ID] (Nov/Dec 2016)
9. What is body effect in MOSFET [ID] (May/June 2016)
10. Give the general condition under which common source amplifier would be used. [ID] (M/J 16).

11. Compare between JFET and MOSFET [D] (Apr/May 2015)

 12. Determine the output impedance of a JFET amplifier shown in fig. Let $g_m = 2 \text{ mA/V}$ and $\lambda = 0$ [ID] (Apr/May 2015)



13. Draw the small signal equivalent model of JFET. [D] (Nov/Dec 2014)

14. Write the characteristics of common source MOSFET amplifier. [ID]

15. Write the characteristics of MOSFET source follower amplifier. [ID]

16. Draw the equivalent circuit of common source MOSFET amplifier. [D]

17. Draw the equivalent circuit of common gate MOSFET amplifier. [D]

18. What are the three types of MOSFET amplifiers [D]

19. Draw the BICMOS Darlington pair configuration [D]

20. List the three basic JFET basic configurations? [D]

21. Write the three FET parameters. [D]

22. Define transconductance. [D]

23. Define drain resistance. [D]

24. Define amplification factor. [D]

25. What are the three types of MOSFET amplifiers [D]

26. Draw the equivalent circuit of CS FET. [D]

27. What do you mean by non unilateral amplifiers [ID]

28. What do you mean by unilateral amplifiers [ID]

29. What are the features of bipolar cascode configuration [D]

30. Give the expression for A_v and A_i for NMOS common gate amplifier [ID]

PART B

[FIRST HALF]

Small Signal Hybrid π equivalent circuit of FET and MOSFET

1. Describe the small signal equivalent circuit of the MOSFET and determine the values of small signal parameters. (13) [D] (April/May 2018)

2. Enumerate on voltage swing Limitations, general conditions under which a source follower amplifier would be used. **(OR)** With a neat diagram explain the source follower amplifier using MOSFET and derive the necessary equations to calculate the voltage gain input and output resistance. **(13) (April/May 2018) [D] (Nov/Dec 2014)**
3. Draw a small signal low frequency model for an FET and Explain. **[D] (6)**
4. Draw the characteristics of JFET and mark its region of operation. **[D] [4]**


Analysis of CS, CD and CG amplifiers using Hybrid π equivalent circuits

5. With a neat diagram small signal analysis of common source amplifier with a source resistance for MOSFET. **(13) [D] (Nov/Dec 2017)**
6. Explain about MOSFET CG amplifier and derive the expression for gain, input impedance and output impedance. **(13) [D] (Nov/Dec 2015. April/May 2017)**
7. Draw the circuit of a basic common source amplifier with voltage divider bias and derive the expression for voltage gain, input impedance and output impedance using small-signal model. **(7) (Nov/Dec 2014, Nov/Dec 2016)**
8. Explain about MOSFET CS amplifier and derive the expression for gain, input impedance and output impedance. **(13)**
9. Explain in detail about voltage swing limitations. **(6)**
10. Compare in detail about CG, CD, CG amplifier. **(7)**
11. Determine the voltage gain of the circuit assuming the following parameters $V_{D0} = 3.3 \text{ V}$, $R_D = 4 \text{ K}\Omega$, $R_{G1} = 10 \text{ K}\Omega$, $R_{G2} = 60 \text{ K}\Omega$, $R_{G1} = 10 \text{ K}\Omega$, $R_{S1} = 4 \text{ K}\Omega$. The transistor parameters are: $V_{TN} = 0.4 \text{ V}$, $K_a = 0.5 \text{ mA/V}^2$, and $\lambda = 0.02 \text{ V}^{-1}$. **(7) [D] (Nov/Dec 2016)**
12. Enumerate in detail and derive expression for voltage gain of CS and CD amplifier under small signal low frequency condition. **(13) [D] (Nov/Dec 2015)**


[SECOND HALF]

Basic FET differential pair

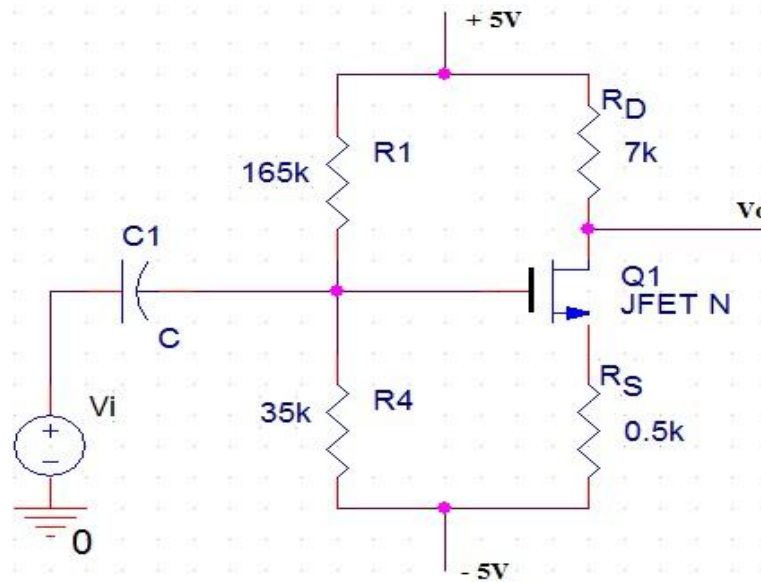13. Derive gain, input and output impedance of common source JFET amplifier with neat diagram and equivalent circuit. **(13) [D] (April/May 2017, Nov/Dec 2014)**
14. Draw a discrete JFET CG amplifier and derive the expression for gain, input impedance and output Impedance small signal equivalent circuit. **(6) [D] (Apr/May 2015)**
15. Determine the current gain of JFET source follower amplifier. **(6) [D] (Apr/May 2015)**
16. Derive a small signal low frequency model for an FET and explain. **(13) [D] (Nov/Dec 2009)**
17. Determine the small signal voltage gain of a common source circuit containing a source resistor. The transistor parameters are $V_{TN}=0.8\text{V}$, $K_n=1\text{mA/V}^2$ and $\lambda=0$ **(15) [D] (May/June 2016)**



 
18. Design a JFET source follower circuit with a specified small voltage gain given $I_{DSS}=12\text{mA}$, $V_p=-4\text{V}$, $\lambda=0.01\text{V}^{-1}$. Determine R_s and I_{DQ} such that the small voltage gain is at least $A_v=0.90$ (15) [D] (May/June 2016)



BiCMOS circuits.

19. Explain the operation of BiMOS cascode amplifier with a neat diagram. [D] (Nov/Dec 2015)

20. Derive the voltage gain of BiCMOS cascode amplifier shown in fig. (13) [D] (Apr/May 2015)

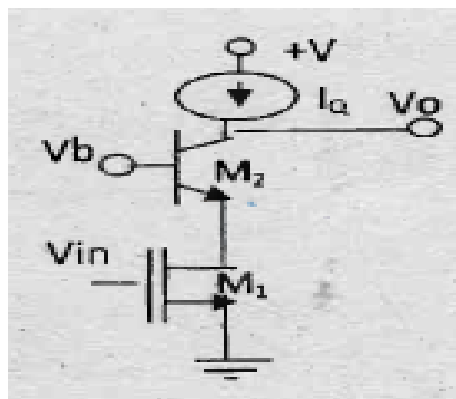

UNIT IV
FREQUENCY RESPONSE OF AMPLIFIERS
PART A


1. Define 3 db frequency? [ID] (April/May 2018)
2. What is beta frequency? [D] (April/May 2018)
3. What is Miller effect? [D] (Nov/Dec 2017)
4. What is Unity gain of amplifier? [ID] (Nov/Dec 2017)
5. Define rise time. Give relation between rise time and bandwidth [ID] (April/May 2017)
6. Draw the hybrid π equivalent circuit of BJT [D] (Nov/Dec 2015, Nov/Dec 16, Apr/May 17)
7. What is the reason for reduction in gain at lower and higher frequencies in case of amplifiers. [ID] (Nov/Dec 2016)
8. Determine the unity gain bandwidth of a FET with parameters, $C_{gd}=10\text{fF}$, $C_{gs}=50\text{fF}$ and $g_m = 1.2 \text{ mA/V}$. [ID] (Nov/Dec 2016)
9. A bipolar transistor has parameter $\beta_o= 150$, $C_{\pi}=2\text{pF}$, $C_{\mu}=0.3\text{pF}$ and is biased at $I_{CQ} = 0.5 \text{ mA}$. Determine the cut off frequency. [ID] (April/May 2016)
10. Find the unity gain bandwidth of a MOSFET whose, $C_{ds} = 1 \text{ pf}$, $C_{gd} = 10 \text{ pF}$, $C_{gs} = 8\text{pF}$ and $g_m = 6 \text{ mA/V}$. [ID] (April/May 2015)
11. The ac schematic of an NMOS common source stage is shown in the fig where part of the biasing circuits has been omitted for simplicity. For the N – channel MOSFET M_1 , the transconductance, $g_m = 1 \text{ mA/V}$, and body effect and channel length modulation effect are to be neglected. Find the lower cutoff frequency. [ID] (April/May 2015)
12. What is the effect of Millers capacitance on the frequency response of an amplifier [D] (Nov/Dec 2014)
13. Relate gain and bandwidth of single and multi-stage amplifier. [ID] (Nov/Dec 2014)
14. The rise time of BJT is 40ns, what is the bandwidth by using this BJT [D] (May/June 2012)
15. Give the equation of overall upper cutoff frequencies and lower cutoff frequencies of multistage amplifier [ID] (May/June /2008)
16. Draw the high frequency model for FET [D] (May/June 2012)
17. What is a miller capacitance of a transistor? [D]
18. Define the frequencies f_T & f_{β} [ID]
19. Draw the frequency response of amplifiers. [D]
20. In an amplifier the maximum voltage gain is 2000, occurs at 2KHz. It falls to 1414 at 10Hz and 50Hz. Find i) B.W ii) Lower and upper cut off frequency. [D]
21. A three stage amplifier has a first stage voltage gain of 100, second stage voltage gain is 200 & third stage gain of 400. Find the total voltage gain in db. [ID]
22. What is the bandwidth of an amplifier. [D]
23. What is the relationship between bandwidth and rise time. [ID]
24. Define sag in an amplifier. [ID]

25. What is meant by gain bandwidth product. [ID]
26. Discuss the effect of bypass capacitor on frequency response of amplifier. [ID]
27. Why is not possible to use the h parameters at high frequencies. [D]
28. Give the expression for gain bandwidth product for voltage and current. [D]
29. What do you mean by unity gain frequency? [D]
30. List the various gate capacitances in MOSFET. [D]


PART B
[FIRST HALF]

Frequency response of transistor amplifiers with circuit capacitors

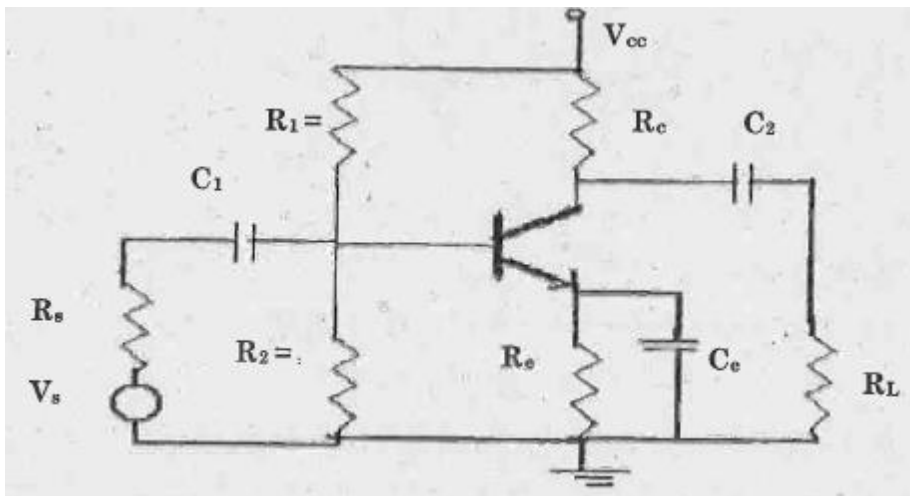
1. With neat sketch, explain hybrid π CE transistor model. Derive the expression for various components in terms of h parameters (13) [D] (April/May 2018, Nov/Dec 2015)
2. Explain the high frequency response of common emitter amplifier and derive the necessary equation to calculate the upper 3 DB frequency. (13) [ID] (Nov/Dec 2017)
3. Determine the low frequency response of the amplifier circuit shown in Fig. Given data's $R_S = 680 \Omega$; $R_1 = 68 \text{ K } \Omega$; $R_2 = 22 \text{ K } \Omega$; $R_e = 1 \text{ K } \Omega$; $V_{cc} = 10 \text{ V}$, $C_1 = C_2 = 0.11 \mu\text{F}$; $C_E = 10 \mu\text{F}$. $R_C = 2.2 \text{ K } \Omega$; $R_L = 10 \text{ K } \Omega$; $\beta = 100$, $h_{ie} = r_{\pi} = 1.1 \text{ k}$ (13) [ID] (April/May 2017)



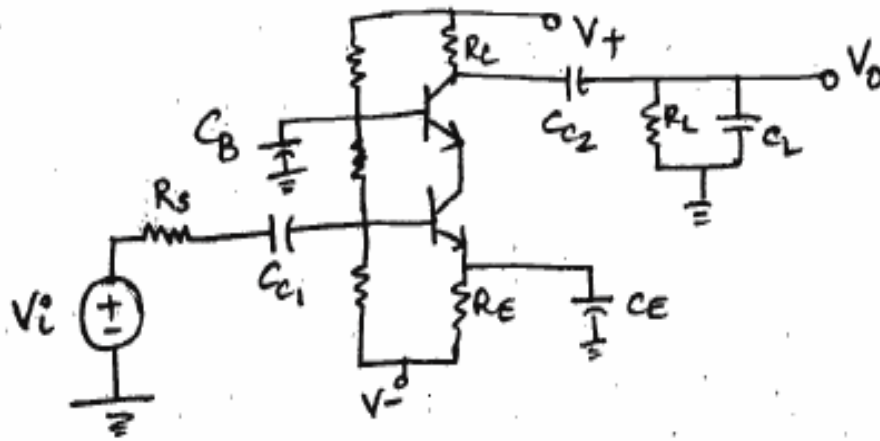
4. Determine the 3 dB frequencies and mid band gain of a cascade circuit. for the figure the parameters are $V^+ = 10 \text{ V}$, $V^- = -10 \text{ V}$, $R_S = 0.1 \text{ k}\Omega$, $R_1 = 42.5 \text{ k}\Omega$, $R_2 = 20.5 \text{ k}\Omega$, $R_3 = 28.3 \text{ k}\Omega$, $R_E = 5.4 \text{ k}\Omega$, $R_C = 5 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, $C_L = 0$. the transistor parameters are $\beta = 150$, $V_{BE(ON)} = 0.7 \text{ V}$, $V_A = \text{infinity}$, $C_{\pi} = 35 \text{ pF}$ and $c_{\mu} = 4 \text{ pF}$ (13) [ID] (May/June 2016)



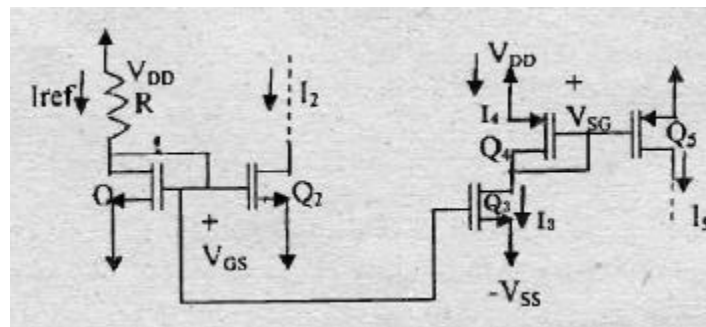5. Explain about the high frequency response of common source and derive the expression for lower cut off frequency and upper cut off frequency [D] (13) (April/May 2014, Nov/Dec 2014)
6. Find the Mid band gain AM and upper 3 - dB frequency hi of a CS amplifier fed with a signal source having an internal resistance $R_{sig} = 100 \text{ K}\Omega$. The Amplifier has $R_G = 4.7 \text{ M}\Omega$, $R_D = R_L = 15 \text{ K}\Omega$, $g_m = 1 \text{ mA/V}$, $r_o = 150 \text{ K}\Omega$, $c_{gs} = 1 \text{ pF}$ and $C_o = 0.4 \text{ pF}$. (15) [ID] (April/May 2017)
7. For the circuit shown in Figure 14, let $V_{DD} = V_{SS} = 1.5 \text{ V}$, $V_{tn} = 0.6 \text{ V}$, $V_{tp} = -0.6 \text{ V}$, all channel lengths = $1 \mu\text{m}$, $K_n = 200 \mu\text{A/V}^2$, $K_p = 80 \mu\text{A/V}^2$ and $\lambda = 0$. For $I_{ref} = 10 \mu\text{A}$, find the widths of all transistors to obtain $I_2 = 60 \mu\text{A}$, $I_3 = 20 \mu\text{A}$ and $I_5 = 80 \mu\text{A}$. It is further required that the voltage at the drain of Q2 be allowed to go down within 0.2 V of the negative supply and voltage at the drain of Q5 be allowed to go up to within 0.2 V of the positive supply. (10) [ID] (April/May 2015)



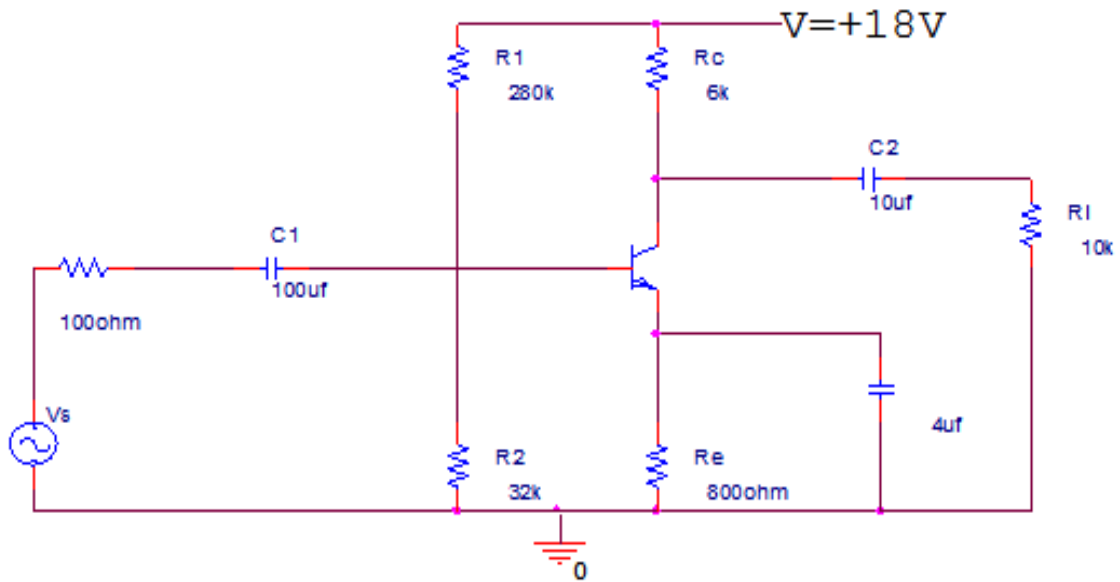8. For the circuit shown find the cut off frequencies due to c_1 and c_2 with $h_{fe} = 100$ and $h_{ie} = k \text{ ohms}$. (6) [D] (April/May 14)




BJT frequency response

9. Derive the expression for cut off frequency of a BJT. (13) [D] (Nov/Dec 2016)

[SECOND HALF]


f_α , f_β and unity gain bandwidth

 10. Explain hybrid π CE short circuit current gain. Derive the expression for $f_\alpha, f_\beta, f_\gamma$. (13) [D] (April/May 15)
11. Derive the expression for $f_\alpha, f_\beta, f_\gamma$ (7) [D] (April/May 2014)
12. Define f_α and f_β and f_T . And also derive for f_α and f_β and f_T with two source terminal and one sink terminal currents as a function of reference current. (13) [ID] (Nov/Dec 2017)
13. Derive expressions for the short circuit current gain of common emitter amplifier at High Frequency. Define alpha cut-off frequency, beta cut-off frequency and transition frequency and derive their values in terms of the circuit parameters. (13) [D] (April/May 2017)
14. Derive for f_β and f_α . (6) [D] (Apr/May 2015)
15. For the circuit shown in below Figure has following parameters: $h_{fe} = 125$, $C_{\pi} = 24$ pF, $C_{\mu} = 3$ pF
 (1) Determine its mid-band gain, upper-cut off frequency. (2) Find the value of C_{c1} , C_{c2} and C_E by assuming lower cut-off frequency of 100 Hz. (10) [D] (Apr/May 2015)




Miller effect

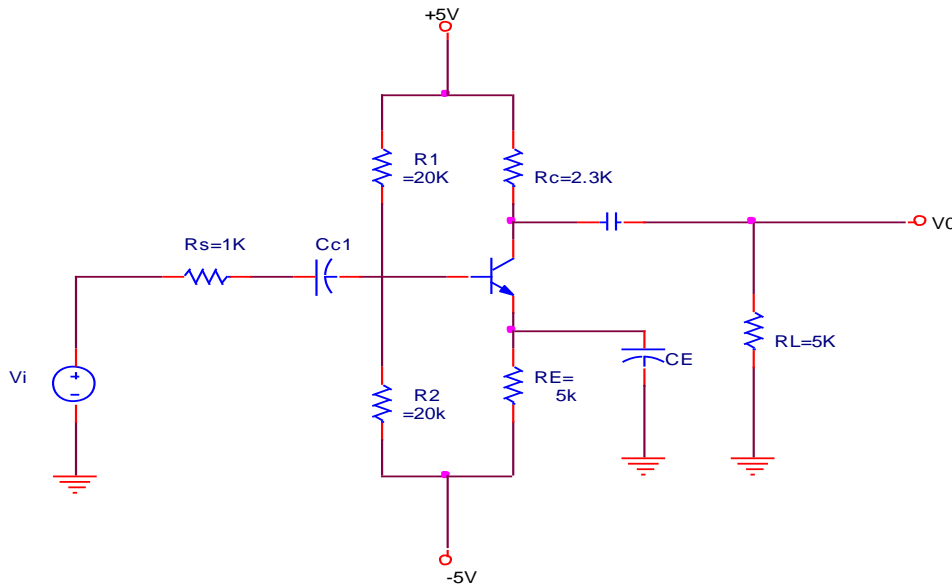16. Explain in detail about the Miller theorem and Miller effect (7) [D]
17. What is multistage amplifier. Explain about the frequency response for multistage amplifier. Derive the expression for overall upper and lower cutoff frequency of the same. (13) [D]
18. The transistor in the figure has parameters $\beta = 125$, $V_{BE(ON)} = 0.7$ V, $V_A = 200$ V, $C_\pi = 24$ pF and $c_\mu = 3$ pF. (13) [ID] (May/June 2016)
- Calculate the miller capacitor
 - Determine the upper 3 dB frequency
 - Determine the small signal mid band voltage gain




Frequency Response of FET, High frequency analysis of CE and MOSFET CS amplifier

 19. Explain the high frequency analysis of JFET with necessary circuit diagram and derive its gain bandwidth product. (13) [D] (April/May 2018)
20. Construct the high frequency equivalent circuit of MOSFET from its geometry and derive the expression for short circuit current gain in the common source configuration. (13) [D] (Nov/Dec 2016)
21. Determine the voltage gain, input impedance, output impedance of CMOS source follower amplifier. (13) [D] (April/May 2015)
22. Consider the circuit of NMOS amplifier with depletion load (shown in below fig) The transistor parameters are $V_{TND} = 0.8$ V, $V_{TNL} = -1.2$ V, $\beta_{nd} = (\mu_{nD}C_{ox}(W/L)) = 500 \mu A/V^2$, $\beta_{nL} = (\mu_{nD}C_{ox}(W/L)) = 50 \mu A/V^2$, $I_{DQ} = 100 \mu A$, $V_{DD} = 5$ V and $\lambda_{nD} = \lambda_{nL} = 0.01$ V⁻¹. (1) Determine V_{GS} such that the Q-point is the mid of the saturation region. (2) Calculate Q-point drain current. (3) Determine the small signal voltage gain. (8) [ID] (April/May 2015)



 23. For the NMOS inverter circuit with saturated load (shown in below), the transistor parameters are: (device data for M_D : $V_{inD} = 1\text{ V}$, $K_{np} = \mu_n C_{ox}(W/L) = 100\ \mu\text{A}/\text{V}^2$, $\lambda_{nD} = 0$ and device data for M_L : $V_{inL} = 1\text{ V}$, $K_{nL} = \mu_n C_{ox}(W/L) = 20\ \mu\text{A}/\text{V}^2$, $\lambda_{nL} = 0$) Draw its voltage-transfer characteristics curve, and mark down its transition points. (6) [ID] (April/May 2015)



UNIT-V

POWER SUPPLIES AND ELECTRONIC DEVICE TESTING

PART A

- How does a MOSFET work as an amplifier? [ID] (April/May 2018)
- Draw the symbols of PMOS and NMOS. [D] (Nov/Dec 2017)
- Why active loads are not used with discrete Circuits? [ID] (Nov/Dec 2016)
- Define CMRR? [D] (Nov/Dec 2016)
- Mention the different types of active loads [D] (Nov/Dec 2015)
- List out the advantages of CMOS differential amplifier over MOS differential amplifier. [D] (A/M '15)
- Comparison between BJT and MOSFET. [D]
- Comparison between capacitor input and LC filter [D]
- State the advantages of π filter. [D]
- State the Disadvantages of π filter. [D]
- Sketch the block schematic of regulated power supply. [D]
- Comparison of shunt and series regulators [D]
- What is the need of SMPS? [D]
- Derive the ripple factor of FWR. [ID]
- What is a bleeder resistor? State its use. [D]

16. Define transformer utilization factor. State its value for half wave rectifier. **[ID]**
17. Define ripple factor **[D]**
18. Derive the ripple factor of HWR. **[ID]**
19. Define peak inverse voltage. **[D]**
20. Define line regulation and load regulation. **[D]**
21. Where is SMPS used? **[D]**
22. What are advantages of SMPS? **[D]**
23. State any two reasons unregulated power supply is not suitable for many applications. **[ID]**
24. How shunt regulator is differentiated from series regulator? **[ID]**
25. Write down the expression of ripple factor of L filter in FWR. **[D]**
26. Draw the full wave bridge rectifier circuit **[D]**
27. Compare the performance of half wave rectifier and full wave rectifier. **[D]**
28. Why is a simple capacitor filter not suitable for heavy loads? **[ID]**
29. Draw the diagram of CLC filter. **[D]**
30. Draw the transistorized series feedback type regulator. **[D]**

PART B
[FIRST HALF]

Half-Wave Rectifier Power Supply

1. Derive the expression for the rectification efficiency, ripple factor, transformer utilization factor, form factor and peak factor of half wave rectifier. **(8) [D]**
2. Draw and explain the working of half wave rectifier. **(8) [D]**

Full-Wave Rectifier Power Supply

3. Draw and explain the working of Full wave rectifier. **(8) [D]**
4. Derive the expression for ripple factor of LC filter with full wave rectifier. **(8) [ID]**
5. Explain the working of FWR with CLC filter and derive for its ripple filter? **[ID] [13]**
6. Derive the expression for the ripple factor of π filter with full wave rectifier. **[ID] [4]**

Voltage regulators - series, shunt and switching Voltage Regulators

7. Draw a neat diagram of a series regulator and explain its working? **(8) [D]**
8. Explain the circuit of voltage regulator and also discuss the short circuit protection mechanism. **(15) [ID]**
9. With a neat diagram explain the operation of transistorized series type voltage regulator **(13) [D]**
10. Draw the circuit and explain the operation of voltage inverter type switching regulator. **[D] (13)**

[SECOND HALF]

Switched mode power supply

11. How output voltage can be regulated with respect to line and load variations using SMPS? (10) [D]
12. Draw the block diagram of a switched mode power supply and explain the operation. State its advantages. (15) [D]

BJT and MOSFET

13. With the necessary diagram explain about CMOS differential amplifier and derive the CMRR. [D] (16) (April/May 2016)
14. Draw and explain the MOSFET Cascode current source circuit and also discuss its advantages. (13) [D] (April/May 2018)
15. Describe the operation of a PMOS amplifier with an enhancement load and a depletion load with necessary diagrams. (13) [D] (April/May 2018)
16. Describe the working principle of Basic MOSFET current source circuit with neat circuit (13) [D]
17. Describe the working principle of Basic MOSFET current mirror circuit with neat circuit (13) [D]
18. With the analysis, explain about MOSFET current steering circuit. (13) [D] (Nov/Dec 2017) (Apr/May'17)
19. Draw and explain the operation of a simple MOSFET amplifier with active load and derive its voltage gain using small signal equivalent circuit. (13) [D] (Nov/Dec 2016)

DC regulated Power supplies

20. Discuss about the electronically regulated d.c. power supplies [8] [D]

*****All The Best*****