

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 21177

B.E./B.Tech. DEGREE EXAMINATION, MAY/JUNE 2014.

Third Semester

Electronics and Communication Engineering

EC 1203 — ELECTRONIC CIRCUITS — I

(Regulation 2008)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. What is operating point of a transistor amplifier?
2. Define stability factor.
3. Why do we use a bypass capacitor shunting the resistor R_E in a common emitter amplifier?
4. Define CMRR. What is the ideal value?
5. Define gain – bandwidth product.
6. Relate rise time and bandwidth.
7. Define power conversion efficiency.
8. What is class C amplifier? State its applications.
9. Distinguish between voltage and current feedback connection.
10. What is the effect of negative feedback on gain and bandwidth?