

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 51224

B.E./B.Tech. DEGREE EXAMINATION, NOVEMBER/DECEMBER 2013.

Sixth Semester

Electronics and Communication Engineering

EC 1354 – VLSI DESIGN

(Common to Electrical and Electronics Engineering)

(Regulation 2008)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. Define threshold voltage of MOS transistor.
2. Draw small signal model for an MOS transistor.
3. Give the expression for inductance of a conductor on a chip.
4. Define delay time.
5. What do you mean by super buffer?
6. What is stick diagram?
7. Develop block diagram of 4:1 MUX using instanced 2:1 MUX.
8. Write verilog behavioural description of a positive edge triggered D flip flop.
9. Distinguish between behavioural modeling and data flow modeling.
10. What is test bench?

PART B — (5 × 16 = 80 marks)

11. (a) Discuss in detail about second order effects of MOS transistor. (16)

Or

- (b) Explain in detail about basic CMOS technology. (16)

12. (a) (i) An inverter uses FETs with $\beta_n = 2.1\text{mA/v}^2$ and $\beta_p = 1.8\text{mA/v}^2$. The threshold voltages are given as $V_{Tn} = 0.60\text{V}$ and $V_{Tp} = -0.70\text{V}$ and the power supply has a value of $V_{DD} = 5\text{V}$. The parasitic FET capacitance at the output node is estimated to be $C_{FET} = 74\text{fF}$.

- (1) Find the midpoint voltage V_M .
- (2) Find the values of R_n and R_p .
- (3) Calculate the rise and fall times at the output when $C_L = 0$.
- (4) Calculate the rise and fall times at the output when the external load of value $C_L = 115\text{fF}$ is connected to the output. (8)

- (ii) Discuss in detail about DC and transient characteristics of CMOS inverter. (8)

Or

- (b) (i) Sketch the VTC of a CMOS inverter and explain the different regions of operation. (8)

- (ii) Explain the concept of dynamic CMOS design. (8)

13. (a) (i) Explain in detail the capacitance estimation in MOS devices. (8)

- (ii) Write notes on charge sharing. (8)

Or

- (b) (i) Discuss in detail about power dissipation in MOS transistor. (8)

- (ii) Write detailed notes on scaling. (8)

14. (a) (i) Draw the circuits for P_i and G_i needed for a 4 bit Carry look ahead adder in each of the following CMOS technologies:

- (1) Static CMOS; (2) Domino CMOS and (3) TG logic. (10)

- (ii) Construct a 2×2 array multiplier circuit with latching inputs. Write a Verilog description for the above circuit. (6)

Or

- (b) Consider the 4 — bit shift register shown in Figure.1. The data stream D consists of sequential bits d0, d1, d2, and d3. The timing is set such that the first bit d0 enters stage 0 on the first clock edge. On the next rising edge, d1 enters stage 0, while d0 moves to stage 1, and so on.
- Write a Verilog description of the shift register using DFF modules as primitives.
 - Select a CMOS design techniques for the DFFs and use it to construct the circuit.
 - Now write a verilog description of the shift registers using nMOS and pMOS primitives.

 


fig. 1

15. (a) Explain in detail about hierarchical modeling concepts with suitable examples in VHDL. (16)

Or

- Explain the Task and functions in VHDL with an examples. (8)
- Briefly explain dataflow and behavioural level modeling in VHDL. (8)