

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 80436

B.E./B.Tech. DEGREE EXAMINATIONS, NOVEMBER/DECEMBER 2021.

Second Semester

Electronics and Communication Engineering

EC 2151/EC 25/10144 EC 205/080290007/EE 1152 – ELECTRIC CIRCUITS AND
ELECTRON DEVICES

(Common to Computer Science and Engineering, Biomedical Engineering, Medical
Electronics Engineering and Information Technology)

(Regulations 2008/2010)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. State Kirchoff's voltage law.
2. State Superposition theorem.
3. Draw the phasor diagram for a series RL circuit.
4. Draw the frequency response of a single tuned circuit.
5. Draw energy band diagram of semiconductor.
6. Define diffusion capacitance.
7. Define and explain the term 'early effect'.
8. Differentiate between enhancement-type and depletion-type MOSFETs.
9. Mention any two applications of DIAC.
10. What is Photovoltaic effect?

PART B — (5 × 16 = 80 marks)

11. (a) (i) Find the current through each resistor of the circuit shown in Figure. 11(a) using nodal analysis. (10)

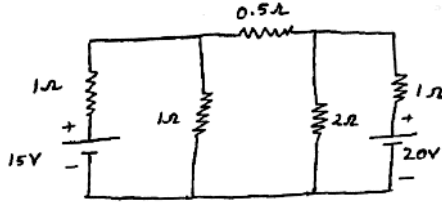


Figure. 11(a)

- (ii) State and prove maximum power transfer theorem. (6)

Or

- (b) (i) Find the Thevenin's equivalent circuit for the network in Figure.11(b) at terminals AB. (10)

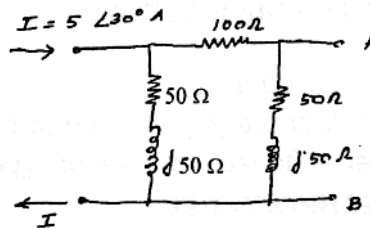


Figure. 11(b)

- (ii) Explain superposition theorem, assuming a suitable circuit. (6)

12. (a) In the RL circuit shown below Fig. Q. 12(a), the output is taken across the inductor.

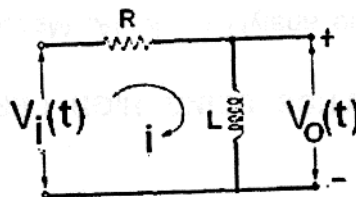


Fig. 12(a)

A pulse input voltage with a pulse width of t_p is applied. Derive the response of the circuit and sketch the output curve. (16)

Or

- (b) Derive expressions for impedance, phase angle, voltages and current in a series RLC resonant circuit. Show their variations graphically with respect to frequency. State how will you find the maximum voltages across L and across C. (16)
13. (a) Derive the PN diode current equation from the quantitative theory of diode currents. (16)

Or

- (b) (i) Sketch and explain the V-I characteristics of zener diodes. (8)
- (ii) Explain briefly the following:
- (1) Avalanche breakdown (4)
- (2) Zener breakdown. (4)
14. (a) Explain with neat diagram the operation of NPN transistor. (16)

Or

- (b) Describe construction and operation of n-channel depletion type MOSFET. (16)
15. (a) (i) With energy band diagram, explain the theory and characteristics of tunnel diode. (10)
- (ii) Write notes on varactor diode. (6)

Or

- (b) (i) Describe the construction, operation and characteristics of UJT. (8)
- (ii) Discuss the operation and characteristics of photodiode. Mention the applications of photodiodes and phototransistors. (8)