

12. (a) (i) Draw hybrid π derive for its parameters. (10)

(ii) Draw CE hybrid π model and CB hybrid π model. (6)

Or

(b) Explain the input and output characteristics of CB configuration using NPN BJT.

13. (a) (i) Explain the working of an channel JEET and hence draw the VI characteristics. (10)

(ii) Compare JEFT and a MOSFET. (6)

Or

(b) (i) How a JEFT small signal high frequency model different from a low frequency model. Explain it briefly. (8)

(ii) Derive the expression for voltage gain and output resistance for a common source JEFT amplifier? (8)

14. (a) Discuss about the stability analysis using frequency response of the loop gain of the feed back amplifier system. Explain all the compensation methods of achieve stability in amplifiers. (16)

Or

(b) Discuss about the following feedback configurations of amplifiers and obtain the feedback factor and closed loop gain.

(i) Shunt – Shunt feed Back.

(ii) Series – Series feed Back. (16)

15. (a) (i) Discuss the operation of one shot multivibrator with relevant waveforms. (8)

(ii) Describe the UJT based sawtooth generator. (8)

Or

(b) Describe the following waveshaping circuits

(i) One level clipper

(ii) Two level clamper

(iii) Sinusoidal to square pulse converter. (4 + 4 + 8)