

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 70429

B.E./B.Tech. DEGREE EXAMINATION, NOVEMBER/DECEMBER 2021.

Third Semester

Electronics and Communication Engineering

EC 6304 — ELECTRONIC CIRCUITS — I

(Regulations 2013)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. List out the three stability factor.
2. Find the collector and base current of circuit given in fig Q.2 $h_{fe} = 80$, $V_{BE(ON)} = 0.7 \text{ V}$.

 


Fig. Q.2

3. What is an ac load line?
4. Draw the small-signal ac equivalent circuit of the BJT.
5. Calculate the output resistance of a source-follower circuit Given that $R_s = 0.75 \text{ k}\Omega$, $r_o = 12.5 \text{ k}\Omega$ and $g_m = 11.3 \text{ mA/V}$.

6. Draw the low frequency equivalent circuit of FET.
7. Find the unit gain bandwidth of MOSFET whose $g_m = 6 \text{ mA/V}$, $C_{gs} = 8 \text{ pF}$, $C_{gd} = 4 \text{ pF}$ and $C_{ds} = \text{pF}$.
8. The ac schematic of an NMOS common-source stage is shown in the Figure Q.8, where part of the biasing circuits has been omitted for simplicity. For the N-channel MOSFET M_1 , the transconductance, $g_m = 1 \text{ mA/V}$, and body effect and channel length modulation effect are to be neglected. Find the lower cutoff frequency.

 


Figure Q.8

9. Mention the different types of active loads.
10. Draw a NMOS current source.

PART B — ($5 \times 13 = 65$ marks)

11. (a) Analyze a BJT with a voltage divider bias circuit, and determine the change in the Q-point with a variation in β when the circuit contains an emitter resistor. Let the biasing resistors be $R_{B1} = 56 \text{ k}\Omega$, $R_{B2} = 12.2 \text{ k}\Omega$, $R_C = 2 \text{ k}\Omega$, $R_E = 0.4 \text{ k}\Omega$, $V_{CC} = 10 \text{ V}$, $V_{EE(ON)} = 0.7 \text{ V}$ and $\beta = 100$.

Or

- (b) Consider the circuit shown below in Fig. Q.11(b) with transistor parameters $I_{DSS} = 12\text{mA}$, $V_P = -4\text{V}$, and $\lambda = 0.008\text{V}^{-1}$. Determine the small-signal voltage gain $A_V = v_o/v_i$.

 


Fig. Q.11(b)

12. (a) Draw the circuit diagram of a Common Emitter amplifier with voltage divider bias, coupling capacitor and bypass capacitor. With the help of small-signal equivalent circuit, obtain the expression for voltage gain, current gain, input and output impedance. (13)

Or

- (b) (i) With relevant circuit diagrams, explain the differential amplifier applied with common mode voltage and differential mode voltage. (8)
- (ii) Draw the h-parameter model of Common emitter NPN transistor and obtain its h-parameters. (5)
13. (a) Derive gain, input and output impedance of common source JFET amplifier with neat diagram and equivalent circuit. (13)

Or

- (b) Draw a common Gate MOSFET amplifier and derive for A_v , A_i and R_i using small signal equivalent circuit.

14. (a) (i) For the circuit shown in Figure Q.14(a)(i), let $V_{DD} = V_{SS} = 1.5 \text{ V}$, $V_{tn} = 0.6 \text{ V}$, $V_{tp} = -0.6 \text{ V}$, all channel lengths = $1 \mu\text{m}$, $K_n = 200 \mu\text{A/V}^2$, $K_p = 80 \mu\text{A/V}^2$ and $\lambda = 0$. For $I_{ref} = 10 \mu\text{A}$, find the widths of all transistors to obtain $I_2 = 60 \mu\text{A}$, $I_3 = 20 \mu\text{A}$ and $I_5 = 80 \mu\text{A}$. It is further required that the voltage at the drain of Q_2 be allowed to go down within 0.2 V of the negative supply and voltage at the drain of Q_5 be allowed to go up to within 0.2 V of the positive supply. (8)

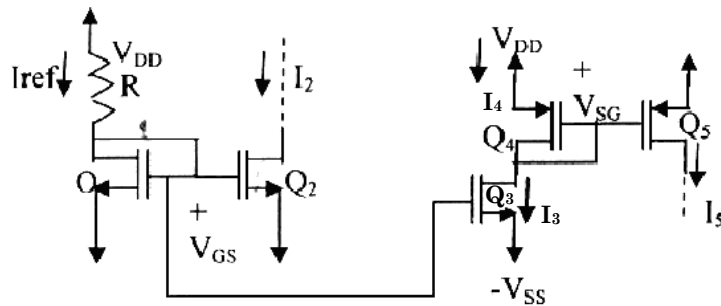


Figure Q.14(a)(i)

- (ii) For the NMOS inverter circuit with saturated load (vide Figure Q.14(a)(ii)), the transistor parameters are: (device data for M_D : $V_{tn_D} = 1 \text{ V}$, $K_{n_D} = \mu_n C_{ox}(W/L) = 100 \mu\text{A/V}^2$, $\lambda_{n_D} = 0$ and device data for M_L : $V_{tn_L} = 1 \text{ V}$, $K_{n_L} = \mu_n C_{ox}(W/L) = 20 \mu\text{A/V}^2$ and $\lambda_{n_L} = 0$). Draw its voltage-transfer characteristics curve, and mark down its transition points. (3)

 


Figure Q.14(a)(ii)

- (iii) For CMOS differential amplifier with NMOS differential pair and PMOS current source as active load. Given $I_{DQ} = 500 \mu\text{A}$, $(W/L)_{\text{NMOS}} = 5$, $\mu_n C_{ox} = 115 \mu\text{A/V}^2$, $\mu_p C_{ox} = 30 \mu\text{A/V}^2$, $\lambda_n = 0.01 \text{V}^{-1}$, $\lambda_p = 0.02 \text{V}^{-1}$. Find differential mode voltage gain. (2)

Or

- (b) (i) Consider the circuit of NMOS amplifier with depletion load (Vide Figure Q.14(b)(i)). The transistor parameters are $V_{TND} = 0.8 \text{V}$, $V_{TNL} = -1.2 \text{V}$, $\beta_{nD} = (\mu_{nD} C_{ox} (W/L)) = 500 \mu\text{A/V}^2$, $\beta_{nL} = (\mu_{nL} C_{ox} (W/L)) = 50 \mu\text{A/V}^2$, $I_{DQ} = 100 \mu\text{A}$, $V_{DD} = 5 \text{V}$ and $\lambda_{nD} = \lambda_{nL} = 0.01 \text{V}^{-1}$. (1) Determine V_{GS} such that the Q-point is the mid of the saturation region. (2) Calculate Q-point drain current. (3) Determine the small signal voltage gain. (6)

 


Figure Q.14(b)(i)

- (ii) Determine the voltage gain, input impedance, output impedance of CMOS source follower amplifier. (7)
15. (a) Discuss the operation of MOS differential Amplifier with active and derive for CMRR.

Or

- (b) Explain in detail the operation of CMOS common source and source follower with neat diagram and derive for A_v .

PART C — (1 × 15 = 15 marks)

16. (a) Find the Midband gain A_M and upper 3 — dB frequency f_H of a CS amplifier fed with a signal source having an internal resistance $R_{sig} = 100 \text{K}\Omega$. The Amplifier has $R_G = 4.7 \text{M}\Omega$, $R_D = R_L = 15 \text{K}\Omega$, $g_m = 1 \text{mA/V}$, $r_o = 150 \text{K}\Omega$, $C_{gs} = 1 \text{pF}$ and $C_{gd} = 0.4 \text{pF}$. (15)

Or

- (b) Calculate the input and output resistance of the emitter-follower circuit shown in Fig. Q.16(b). Assume $R_s = 0.5 \text{ k}\Omega$, $r_\pi = 3.28 \text{ K}\Omega$, $\beta = 100$ and $r_o = 100 \text{ K}\Omega$.

 


Fig. Q.16 (b)