

Reg. No.:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code : 50955**

ECE-1

B.E./B.Tech. DEGREE EXAMINATIONS, APRIL/MAY 2024.

Second Semester

Electronics and Communication Engineering

EC 3251 — CIRCUIT ANALYSIS

(Common to : Electronics and Telecommunication Engineering)

(Regulations 2021)


Time : Three hours

Maximum : 100 marks

Answer ALL questions.


PART A — (10 × 2 = 20 marks)

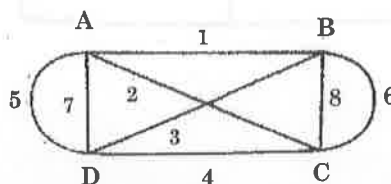1. State Kirchoff's current law.
2. Define Independent source.
3. State Maximum power transfer theorem.
4. State the dual elements for the following.
  - (a) Resistance
  - (b) Capacitance
  - (c) Inductance
  - (d) Mesh current
5. Write the expression for the total admittance of Y1 and Y2 in series and parallel combination.
6. What is the expression for average power in a single phase circuit? Explain the terms involved.
7. An RLC series circuit has  $R = 10\Omega$ ,  $X_C = 62.833 \Omega$ . Find the value of L for resonance at 50HZ.
8. Compare the series and parallel resonant circuit.
9. Define Link.
10. For the network graph shown in the figure, show a tree and the corresponding links.



PART B — (5 × 13 = 65 marks)

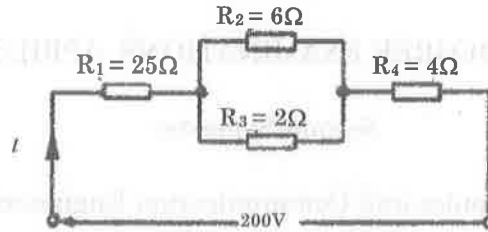11. (a) (i) For the series-parallel arrangement shown in Figure, find  
 (1) the supply current,  
 (2) the current flowing through each resistor and  
 (3) the potential difference across each resistor. (10)





- (ii) Draw the Norton's equivalent circuit. (3)

Or


- (b) (i) Three resistances of values  $2\Omega$ ,  $3\Omega$  and  $5\Omega$  are connected in series across  $20V$ , D.C Supply. Calculate  
 (1) equivalent resistance of the circuit  
 (2) the total current of the circuit  
 (3) the voltage drop across each resistor and  
 (4) the power dissipated in each resistor. (8)
- (ii) A lamp can work on  $50$  volt mains taking  $2$  amps. What value of the resistance must be connected in series with it so that it can be operated from  $200$  volt mains giving the same power? (5)

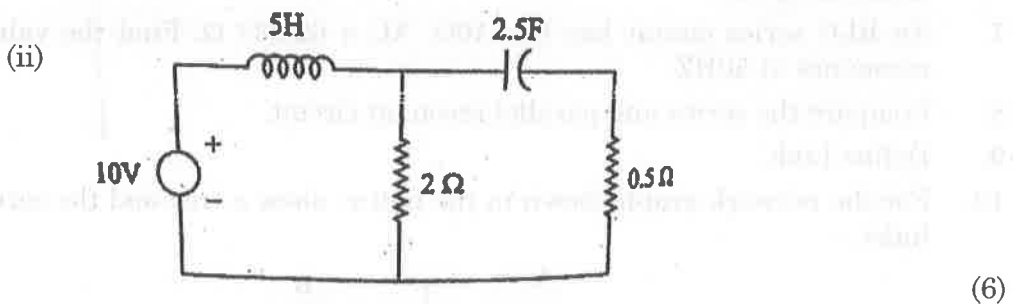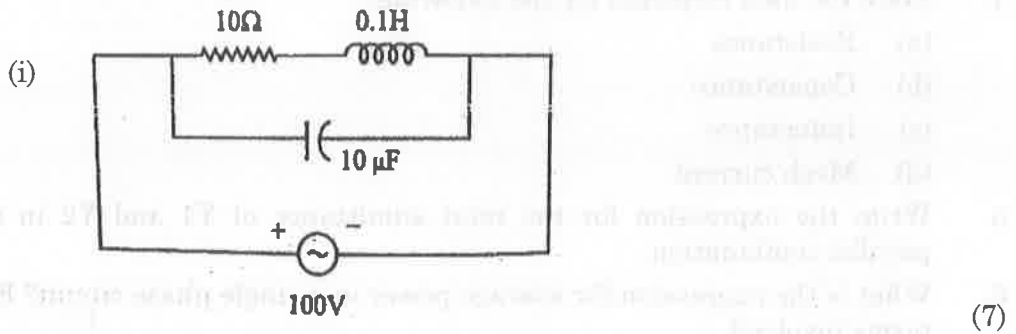12. (a) Draw the dual network of network shown below.



Or

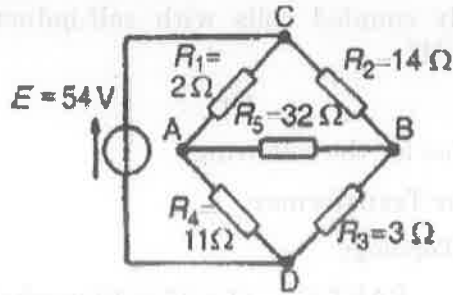- (b) (i) Wheatstone Bridge network is shown in Figure. Calculate the current flowing in the  $32\Omega$  resistor, and its direction, using Thévenin's theorem, Assume the source of e.m.f. to have negligible resistance. (10)



- (ii) A star-connected load consists of three identical coils each of resistance  $30\Omega$  and inductance  $127.3\text{ mH}$ . If the line current is  $5.08\text{ A}$ , calculate the line voltage if the supply frequency is  $50\text{ Hz}$ . (3)
13. (a) A pure inductance of  $1.273\text{ mH}$  is connected in series with a pure resistance of  $30\Omega$ . If the frequency of the sinusoidal supply is  $5\text{ kHz}$  and the potential difference across the  $30\Omega$  resistor is  $6\text{ V}$ , determine the value of the supply voltage and the voltage across the  $1.273\text{ mH}$  inductance. Draw the phasor diagram. (13)

Or

- (b) Two impedances  $(15 - j10)\Omega$  and  $(10 + j15)\Omega$  are connected in parallel. The supply voltage is  $200\text{ V}$ ,  $50\text{ Hz}$ . Calculate
- the admittance,
  - conductance,
  - susceptance of the combined circuit,
  - total current,
  - total power factor. (13)
14. (a) A series L-R-C circuit has a sinusoidal input voltage of maximum value  $12\text{ V}$ . If inductance,  $L = 20\text{ mH}$ , resistance,  $R = 80\Omega$ , and capacitance,  $C = 400\text{ nF}$ , determine
- the resonant frequency,
  - the value of the potential difference across the capacitor at the resonant frequency,
  - the frequency at which the potential difference across the capacitor is a maximum, and
  - the value of the maximum voltage across the capacitor. (13)

Or

- (b) A coil of inductance  $5\text{ mH}$  and resistance  $10\Omega$  is connected in parallel with a  $250\text{ nF}$  capacitor across a  $50\text{ V}$  variable-frequency supply. Determine
- the resonant frequency,
  - the dynamic resistance,
  - the current at resonance, and
  - the circuit Q-factor at resonance. (13)


15. (a) (i) Derive the formula for mutual inductance in terms of coefficient of coupling and self-inductance. (10)
- (ii) What is the maximum possible mutual inductance of two inductively coupled coils with self-inductances  $L_1 = 25\text{mH}$  and  $L_2 = 100\text{mH}$ ? (3)

Or

- (b) Write short notes for the following :
- (i) The Linear Transformer (8)
- (ii) Network Topology. (5)

PART C — (1 × 15 = 15 marks)

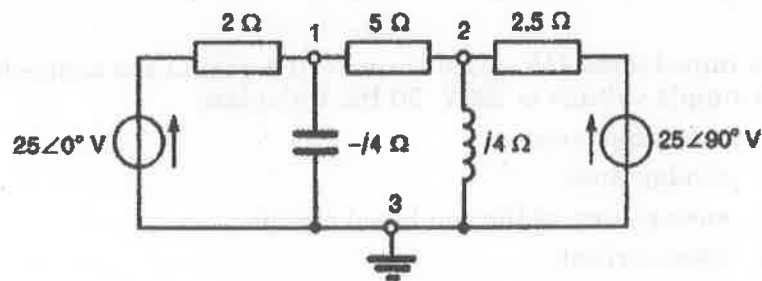16. (a) In the network of figure shown here, use nodal analysis to determine
- (i) the voltage at nodes 1 and 2.
- (ii) the current in the  $j4\ \Omega$  inductance,
- (iii) the current in the  $5\ \Omega$  resistance, and
- (iv) the magnitude of the active power dissipated in the  $2.5\ \Omega$  resistance. (15)



Or

- (b) For the a.c. network shown in Figure determine, using mesh-current analysis,
- (i) the mesh currents  $I_1$  and  $I_2$
- (ii) the current flowing in the capacitor, and
- (iii) the active power delivered by the  $100\ \angle 0^\circ$  V voltage source. (15)

